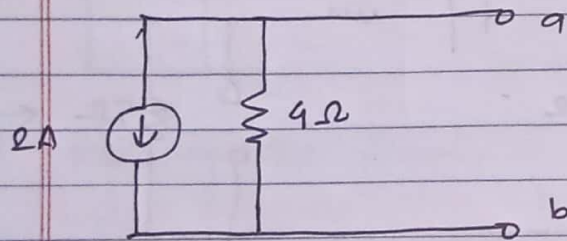




$$I_N = \frac{8V}{4} = 2A$$

$$R_N = R_{TH} = 4\Omega$$



Theremin's
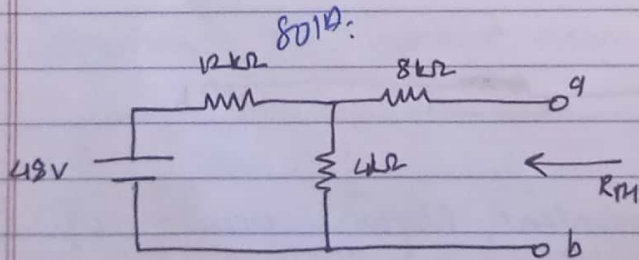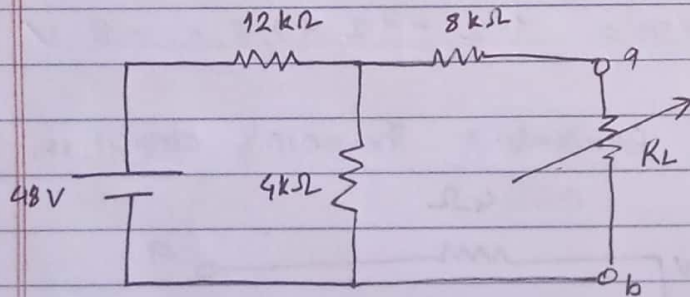
<Num.No. 57> Find equivalent circuit terminals a-b.




Finding R_{TH} ,

$$R_{TH} = (12 \parallel 4) + 8$$

$$= \left(\frac{12 \times 4}{12 + 4} \right) + 8$$

$$\therefore R_{TH} = 11k\Omega$$

Finding V_{TH} ,

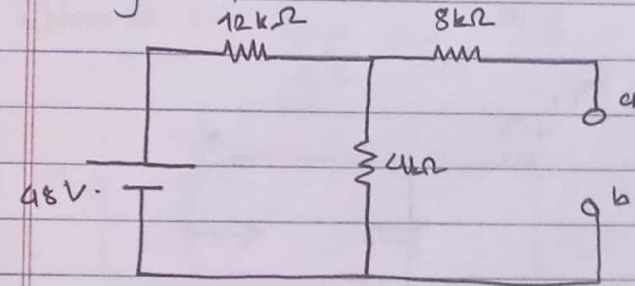


$$R_{eq} = 16$$

$$I_{TH} = \frac{V}{R_{eq}} = \frac{48}{16} = 3mA$$


Thus,

$$V_{a-b} = V_{TH} = 3 \times 4 = 12V$$

Theremin's equivalent theorem,

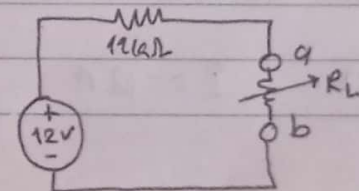


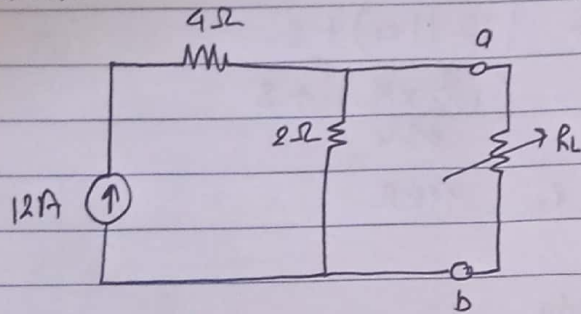(Num. No. 58): Find the Thevenin's equivalent circuit.




Sol/D:

Finding R_{Th} ,

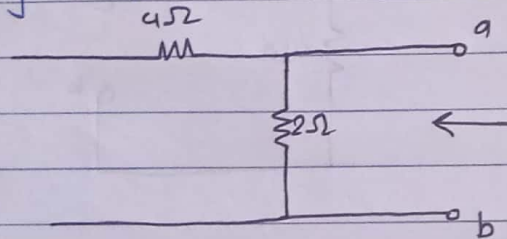

$$R_{Th} = 2\Omega$$


Finding V_{Th} ,

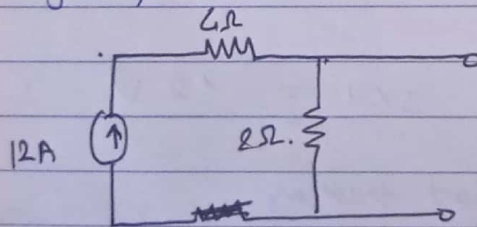


$$R_{eq} = 6\Omega \quad I = 12A \quad \therefore V_{Th} = 72V$$

$$\therefore V_{Th} = V_{oc} = \frac{2 \times 72}{6} = 24V$$

The equivalent circuit is,

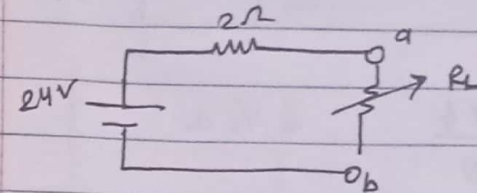


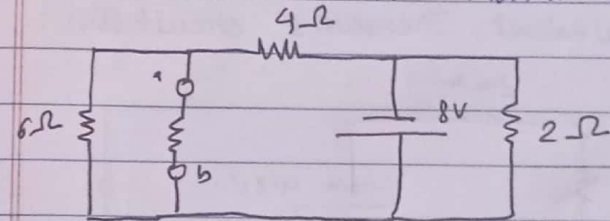(Num. No. 59): Find the Norton's equivalent circuit.




Sol/D:

Finding R_{Th} ,

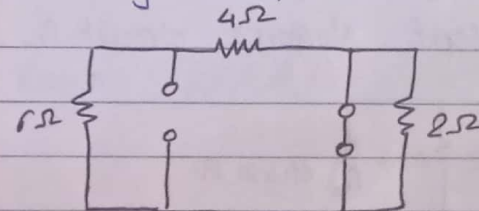


$$R_{Th} = 4 \parallel 6 = \frac{4 \times 6}{10} = 2.4\Omega$$

Finding V_{Th} ,

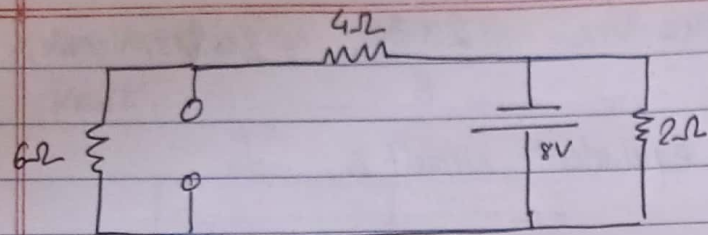


$$V_{th} = \frac{8 \times 6}{10} = \frac{48}{10} = 4.8 \text{ V.}$$


The equivalent Thevenin's circuit is.

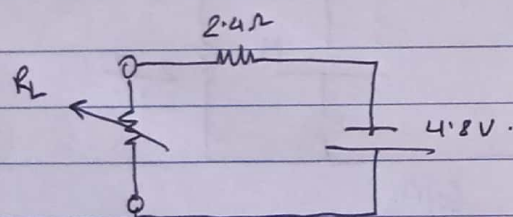


The equivalent Norton's circuit is.

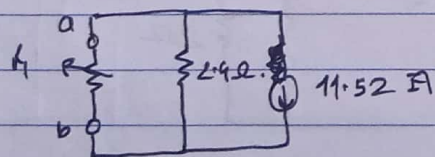

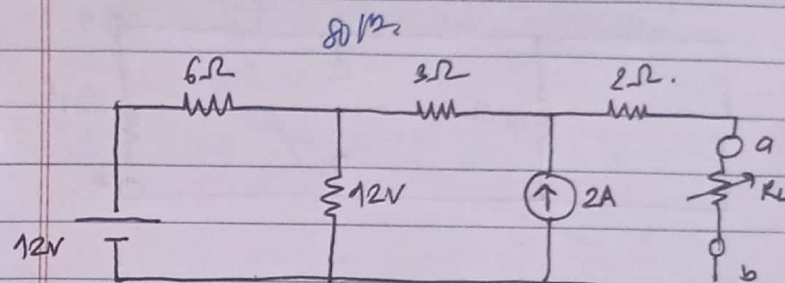Q. No. 60: Find the value of R_L for maximum power transfer in the circuit. Find P_{max} .




Finding R_{th} ,

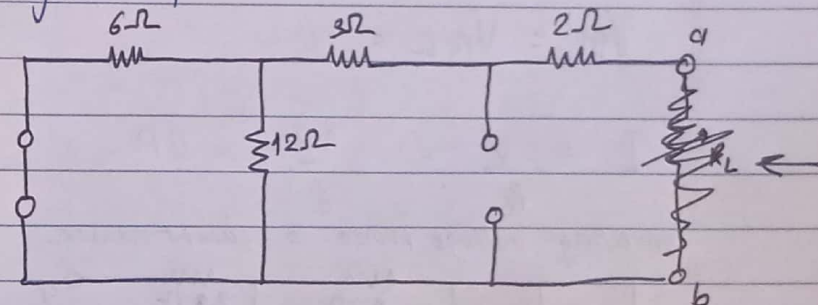

$$\begin{aligned} R_{th} &= \left(\frac{1}{\frac{1}{2A} + \frac{1}{12V}} \right) + 6 \\ &= \frac{5 \times 12}{17} + 6 = \frac{60 + 102}{17} = \frac{162}{17} = 9.52 \Omega. \end{aligned}$$

Finding V_{TH} ,

Considering ~~12 V~~ voltage source,

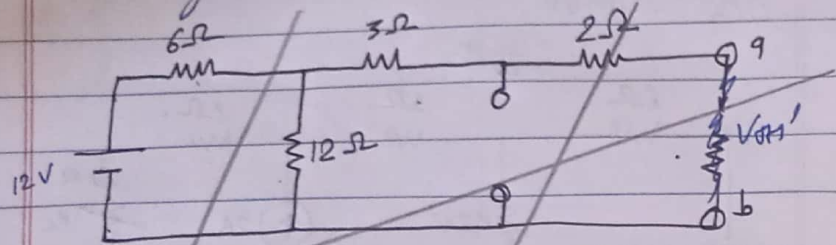


$$R_{eq} = 6 + 12 = 18 \Omega$$


$$V_{TH}' = V_{12\Omega} =$$

$$I = \frac{V}{R_s} = \frac{12}{6} = 2A$$

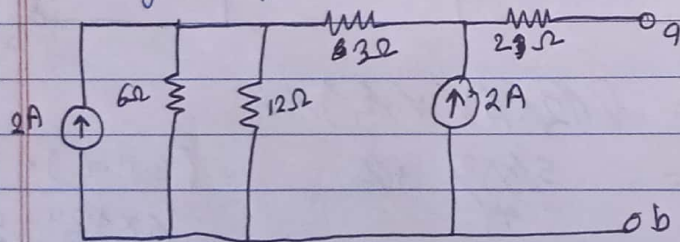
Converting voltage source to current source.




$$R' = 6 || 12 = \frac{6 \times 12}{6+12} = 4 \Omega$$

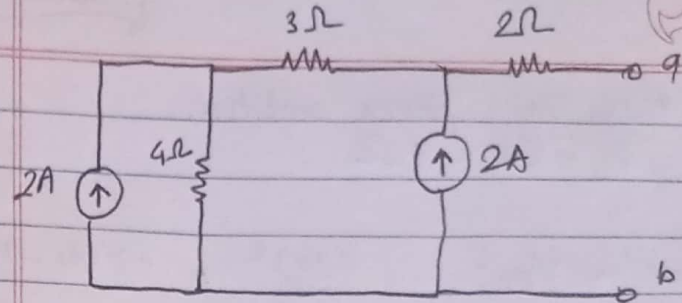

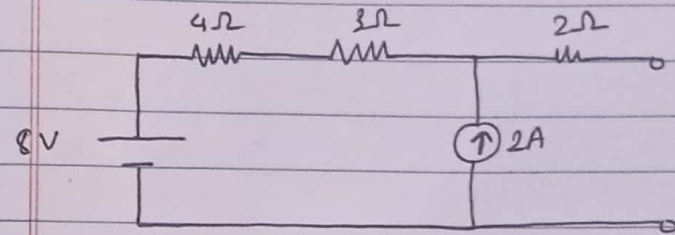
Converting 2A current to voltage source,
 $V = IR = 8V$



Converting 8V voltage to current source.

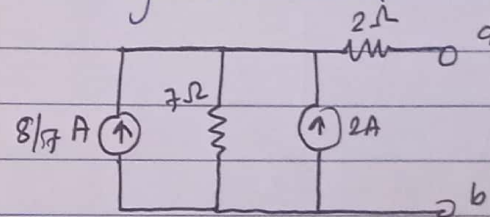
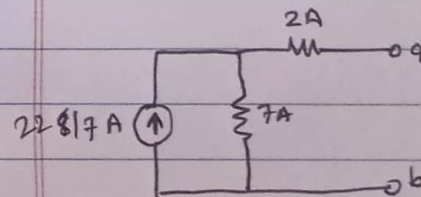
$$I = \left(\frac{8}{7} + 2 \right) = \frac{22}{7} A$$



$$V_{TH} = V_{7\Omega} = \frac{22}{7} \times 7 = 22V$$

For maximum power condition,
 $R_L = R_{TH} = 9 \Omega$.

$$\therefore P_{max} = \frac{V_{TH}^2}{4 \times R_L} = \frac{(22)^2}{4 \times 9} = 13.44 \text{ W}.$$