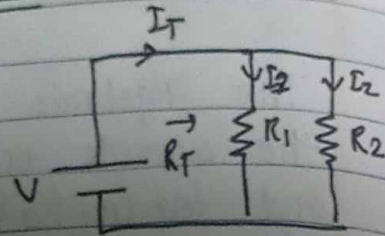


Current Divider Rule:

We know

$$\text{Source Current } (I_s) = \frac{V}{R_T}$$



The voltage 'V' is the same across the parallel elements

$$V = I_1 R_1 = I_2 R_2 \quad \dots [I_1 R_1]$$


$$\text{or, } I_T R_T = I_1 R_1 = I_2 R_2$$

$$\therefore I_x = I_T \times \frac{R_T}{R_x}$$

The current through any branch of a parallel resistive network is equal to the parallel network total resistance of the parallel network divided by the resistor of interest and multiplied by the total amount entering the parallel configuration.

<Num. No. 23> \Rightarrow In numerical copy.

Voltage Source in Parallel

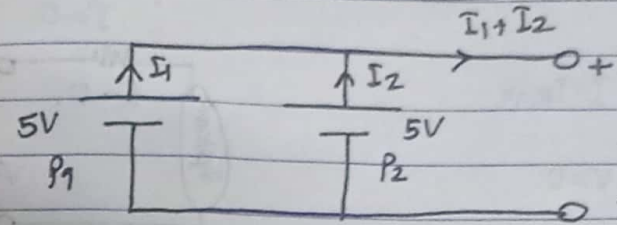

$$\text{Here, } P_1 = I_1 \times V_1$$

$$P_2 = I_2 \times V_2$$

So,

$$P_T = (I_1 + I_2) \times V = 2 \text{ IV} \quad (I_1 = I_2) \\ = 2P$$

In parallel, the battery's connecting must have same voltage to prevent charging and discharging.

*> Short Circuit:


$$\text{Here, } R_4 = 0$$

So,


$$R' = \frac{R_3 R_4}{R_3 + R_4} = 0$$

$$R'' = \frac{R' R_2}{R' + R_2} = 0$$

$$R''' = \frac{R'' R_1}{R'' + R_1} = 0$$

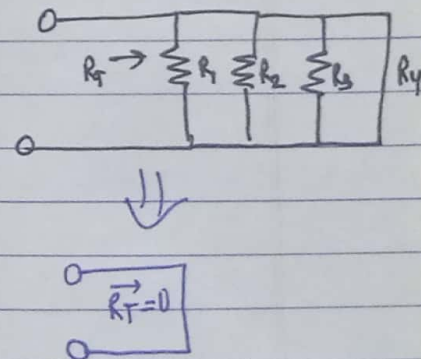


x Closed circuit

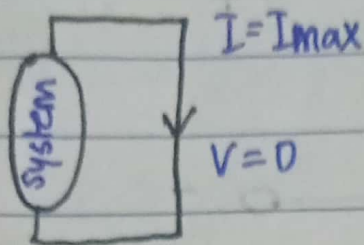

In closed circuit,
current is maximum.
and no voltage if
unresistive.

* Open circuit
 $I = 0$

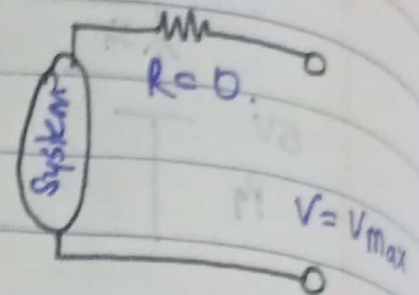

In open circuit,
current is zero
and the voltage
is maximum

< Num. No: 24/25/26/27/28 > \Rightarrow In numerical copy.

