

(X) Notes: (Note copy content)


When to use mesh analysis or node analysis

(i): If number of nodes = number of mesh, we can use any method

(ii) If number of nodes less than number of mesh, we use nodal analysis.

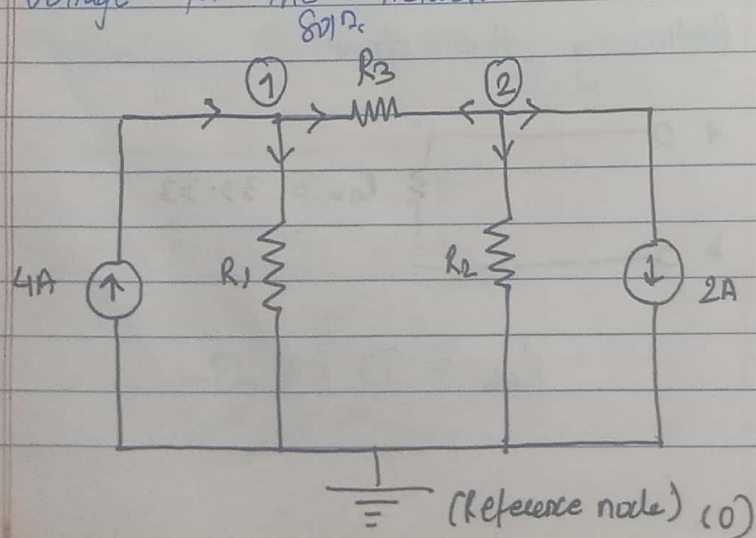(iii) If number of nodes more than number of mesh, we use mesh analysis.

<Num.No.43>: Determine the nodal voltage for the network.



Given,

$$R_1 = 2\Omega$$

$$R_2 = 6\Omega$$

$$R_3 = 12\Omega$$

Now, at node 1, applying KCL,

$$4 = \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_3}$$

$$\text{or, } 4 = \frac{V_1}{2} + \frac{V_1 - V_2}{12}$$

$$\text{or, } 4 = \frac{V_1}{2} + \frac{V_1}{12} - \frac{V_2}{12}$$

$$\text{or, } 4 = \left(\frac{1}{2} + \frac{1}{12} \right) V_1 - \frac{1}{12} V_2$$

$$\text{or, } 4 = \frac{7}{12} V_1 - \frac{V_2}{12}$$

$$\text{or, } 48 = 7V_1 - V_2 \quad \text{--- (i)}$$

At node 2,

$$0 + \frac{V_2}{R_2} + \frac{V_2 - V_1}{R_3} = 0$$

$$\text{or, } 2 + \frac{V_2}{6} + \frac{V_2}{12} - \frac{V_1}{12} = 0$$

$$\text{or, } 2 + \left(\frac{1}{6} + \frac{1}{12} \right) V_2 - \frac{1}{12} V_1 = 0$$

$$\text{or, } 2 + \frac{1}{4} V_2 - \frac{1}{12} V_3 = 0$$

$$\text{or, } -2 = \frac{3V_2 - V_3}{12} \Rightarrow$$


$$\text{or, } 3V_2 - V_3 = -24 \quad \text{--- (ii)}$$

Solving (i) & (ii), we get.


$$V_1 = 6 \text{ V}$$

$$V_2 = -6 \text{ V}$$
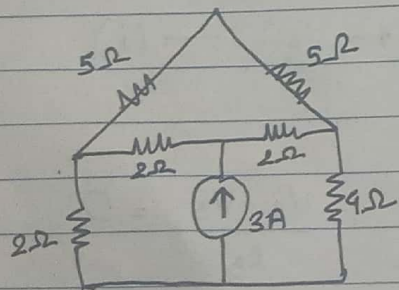
<Num. No. 44>: Using the nodal analysis, find the potential across 4Ω resistor.
SOL:



Redrawing the circuit,

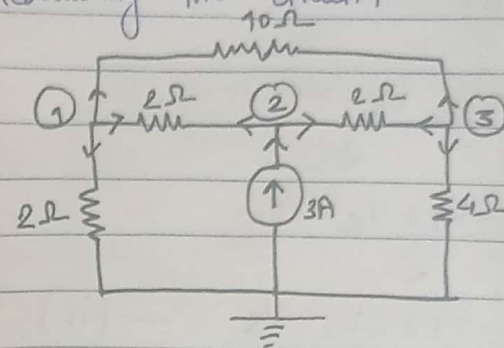

At node 1,

$$\frac{V_1}{2} + \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{10} = 0$$

$$\text{or, } \frac{V_1}{2} + \frac{V_1}{2} - \frac{V_2}{2} + \frac{V_1}{10} - \frac{V_3}{10} = 0$$

$$\text{or, } \frac{V_1}{2} + \frac{V_1}{2} + \frac{V_1}{10} - \frac{V_2}{2} - \frac{V_3}{10} = 0$$

$$\text{or, } \left(\frac{1}{2} + \frac{1}{2} + \frac{1}{10} \right) V_1 - \frac{1}{2} V_2 - \frac{V_3}{10} = 0$$

$$\text{or, } \frac{11V_1}{10} - \frac{V_2}{2} - \frac{V_3}{10} = 0$$

$$\text{or, } \frac{11V_1 - 5V_2 - V_3}{10} = 0$$

$$\text{or, } 11V_1 - 5V_2 - V_3 = 0 \quad \text{--- (i)}$$

At node 2,

$$3 = \frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{2}$$

$$\text{or } 3 = \frac{V_2 - V_1 + V_2 - V_3}{2}$$

$$\text{or } 6 = -V_1 + 2V_2 - V_3 \quad \text{--- (ii)}$$

At node 3,

$$\frac{V_3}{4} + \frac{V_3 - V_2}{2} + \frac{V_3 - V_1}{10} = 0$$

$$\text{or } \frac{V_3}{4} + \frac{V_3 - V_2}{2} + \frac{V_3 - V_1}{10} = 0$$

$$\text{or } -\frac{V_1}{10} - \frac{V_2}{2} + \left(\frac{1}{4} + \frac{1}{2} + \frac{1}{10}\right)V_3 = 0$$


$$\text{or } -\frac{V_1}{10} - \frac{V_2}{2} + \frac{17V_3}{20} = 0$$

$$\text{or } -2V_1 - 10V_2 + 17V_3 = 0 \quad \text{--- (iii)}$$

Solving (i), (ii), (iii), we get,

$$V_3 = V_{4\Omega} = 4.65 \text{ V.}$$

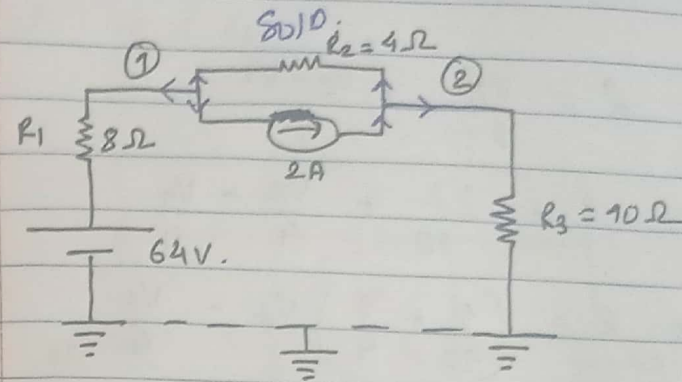(Num. No- 45): Find voltage across the nodes.



(reference node: 0)

At node 1,

$$\frac{V_1 - 64}{8} + 2 + \frac{V_1 - V_2}{4} = 0$$

$$\text{or, } \frac{V_1}{8} - \frac{64}{8} + 2 + \frac{V_1 - V_2}{4} = 0$$

$$\text{or } \frac{V_1}{8} - 8 + 2 + \frac{V_1 - V_2}{4} = 0$$

$$\text{or } \left(\frac{1}{8} + \frac{1}{4}\right)V_1 - \frac{V_2}{4} - 6 = 0$$

$$\text{or, } \frac{3}{8}V_1 - \frac{V_2}{4} = 6$$

$$\text{or, } \frac{3V_1 - 2V_2}{8} = 6$$

$$\text{or, } 3V_1 - 2V_2 = 48 \quad \text{--- (i)}$$

At node 2,

$$2 = \frac{V_2}{10} + \frac{V_2 - V_1}{4}$$

$$\text{or, } 2 = \frac{V_2}{10} + \frac{V_2 - V_1}{4}$$

$$\text{or } 2 = \left(\frac{1}{10} + \frac{1}{4} \right) V_2 - \frac{V_1}{4}$$

$$\text{or, } 2 = \frac{7}{20} V_2 - \frac{V_1}{4}$$

$$2) \quad 2 = \frac{7V_2 - 5V_1}{20}$$

$$\text{or } -5V_1 + 7V_2 = 40 \quad \text{--- (ii)}$$


Solving (i) and (ii), we get.

$$\therefore V_1 = 37.81 \text{ V}$$

$$\therefore V_2 = 32.72 \text{ V.}$$

<Num. No. 46>: Determine the nodal voltage at V_1 & V_2 .


Solⁿ:

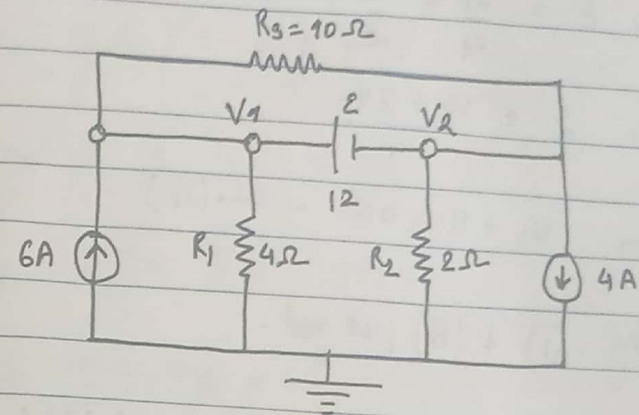

Here,

$$V_1 - V_2 = 12 \quad \text{--- (i)}$$

Redrawing the circuit,

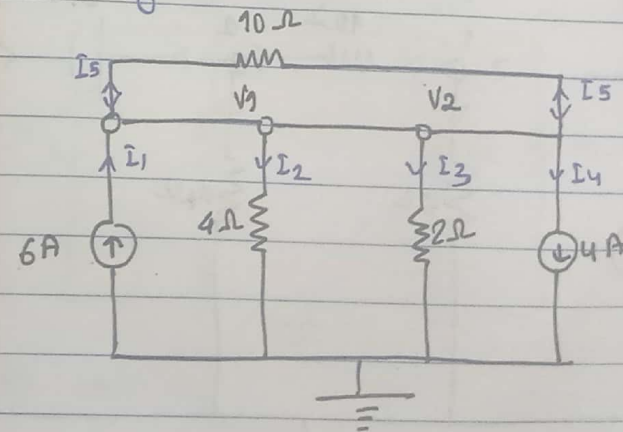

Now,

Now,

$$I_1 = I_2 + I_3 + I_4$$

$$\text{or } 6 = \frac{V_1}{4} + \frac{V_2}{2} + 4$$

$$\text{or } 2 = \frac{V_1 + 2V_2}{4}$$


$$\text{or } V_1 + 2V_2 = 8 \quad \text{--- (ii)}$$

Solving (i) & (ii), we get.

$$\therefore V_1 = 10.67 \text{ V} \quad V_2 = -1.33 \text{ V}$$

Num. No. 47: Find the nodal voltage.

Soln:

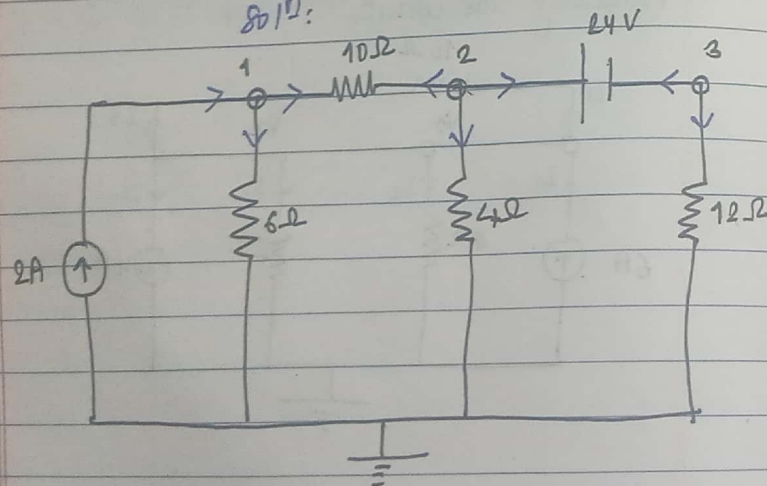

At node 1,

$$2 = \frac{V_1}{6} + \frac{V_1 - V_2}{10}$$

$$\text{or } 2 = \left(\frac{1}{6} + \frac{1}{10} \right) V_1 - \frac{V_2}{10}$$


$$\text{or } 2 = \frac{4V_1}{15} - \frac{V_2}{10}$$

$$\text{or } 2 = \frac{8V_1 - 3V_2}{30}$$

$$\text{or } 8V_1 - 3V_2 = 60 \quad \text{--- (i)}$$

$$V_2 - V_3 = 24 \quad \text{--- (i')}.$$

Redrawing the circuit,

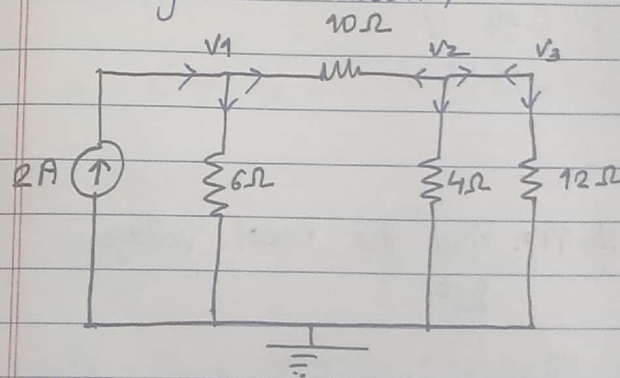

At node 1,

$$2 = \frac{V_1}{6} + \frac{V_1 - V_2}{10}$$

$$\text{or } 8V_1 - 3V_2 = 60 \quad \text{--- (ii)}$$

At node 2,

$$\frac{V_2 - V_1}{10} + \frac{V_2}{4} + \frac{V_3}{12} = 0$$

$$\text{or } \frac{V_2 - V_1}{10} + \frac{V_2}{4} + \frac{V_3}{12} = 0$$

$$\text{or } -\frac{V_1}{10} + \left(\frac{1}{10} + \frac{1}{4} \right) \frac{V_2 + V_3}{12} = 0$$

$$\text{or } -\frac{V_1}{10} + \frac{7V_2 + V_3}{20} = 0$$

$$\text{or } -6V_1 + 7V_2 + V_3 = 0 \quad \text{--- (iii)}$$

Solving (i), (ii) & (iii), we get.


$$V_1 = 10.10 \text{ V}$$

$$V_2 = 6.94 \text{ V}$$

$$V_3 = -17.05 \text{ V.}$$

<Num. No. 47>: Find the nodal voltage.

Sol:

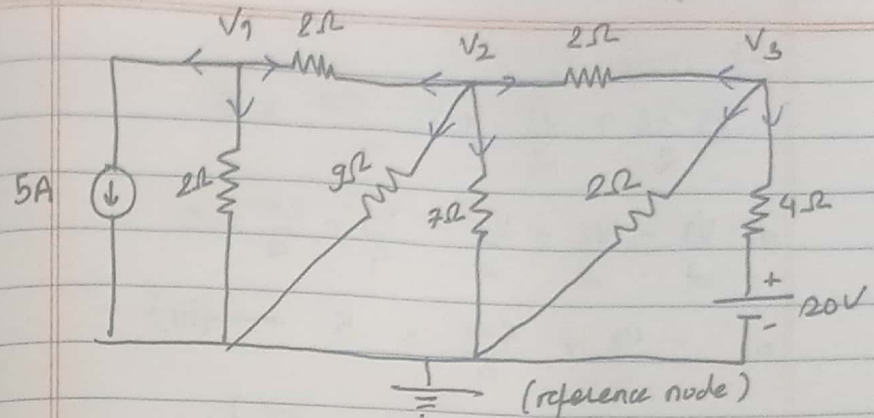

At node 1,

$$5 + \frac{V_1}{2} + \frac{V_1 - V_2}{2} = 0$$

$$\text{or } 5 + \frac{V_1}{2} + \frac{V_1 - V_2}{2} = 0$$

$$\text{or } V_1 - \frac{V_2}{2} = -5$$

$$\text{or } 2V_1 - V_2 = -10 \quad \text{--- (i)}$$

At node 2,

$$\frac{V_2 - V_1}{2} + \frac{V_2}{9} + \frac{V_2}{7} + \frac{V_2 - V_3}{2} = 0$$

$$\text{or } \frac{V_2 - V_1}{2} + \frac{V_2}{9} + \frac{V_2}{7} + \frac{V_2 - V_3}{2} = 0$$

$$\text{or } -\frac{V_1}{2} + \left(\frac{1}{2} + \frac{1}{9} + \frac{1}{7} + \frac{1}{2} \right) \frac{V_2 - V_3}{2} = 0$$

$$\text{or } -\frac{V_1}{2} + \frac{79V_2 - V_3}{63} = 0 \quad \text{or } -63V_1 + 79V_2 - 63V_3 = 0 \quad \text{--- (ii)}$$

At node 3,

$$\frac{V_3 - V_2}{2} + \frac{V_3}{2} + \frac{V_3 - 20}{4} = 0$$

$$\text{or, } \frac{V_3}{2} - \frac{V_2}{2} + \frac{V_3}{2} + \frac{V_3}{4} - \frac{20}{4} = 0$$

$$\text{or, } -\frac{V_2}{2} + \frac{5V_3}{4} = 5 \quad \text{--- (iii)}$$

$$\text{or, } -2V_2 + 5V_3 = 20 \quad \text{--- (iii')}$$

Solving (i), (ii), (iii'), we get.