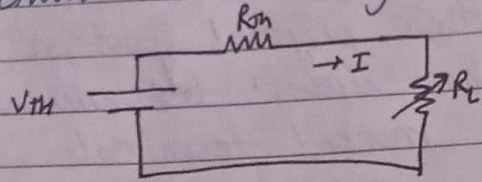


<Num. No. 57/58/59 : In numericals copy>

## # Maximum Power Transfer Theorem:


A load will receive maximum power from a linear bilateral DC network. When its total resistance value is exactly equal to Thevenin's resistance of a network as seen by the load.




$$I = \frac{V_{th}}{R_{th} + R_L}$$

From the network, maximum power delivered when  $R_L = R_{th}$

For Norton's circuit,

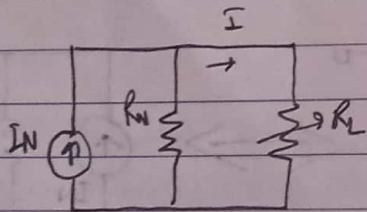

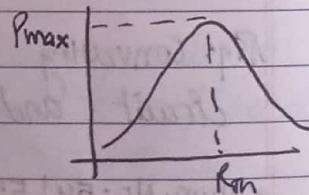From figure, maximum power delivered when  $R_L = R_{th}$ .



Now,

$$P = I^2 R_L = \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 R_L$$

For power to be maximum,

$$\frac{dP}{dR_L} = 0 \quad \text{or,} \quad \frac{d}{dR_L} \left\{ \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 R_L \right\} = 0$$

$$\text{or,} \quad \frac{(V_{th})^2}{(R_{th} + R_L)^2} \frac{dR_L}{dR_L} + R_L \cdot \frac{d}{dR_L} \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 = 0$$

$$\text{or,} \quad \frac{(V_{th})^2}{(R_{th} + R_L)^2} + R_L \cdot V_{th}^2 \times \frac{d(R_{th} + R_L)^{-2}}{dR_L} = 0$$

$$\text{or,} \quad \frac{(V_{th})^2}{(R_{th} + R_L)^2} + R_L \cdot V_{th}^2 \cdot \frac{-2}{(R_{th} + R_L)^3} = 0$$

$$\text{or,} \quad \frac{(V_{th})^2}{(R_{th} + R_L)^2} = \frac{2 R_L \cdot V_{th}^2}{(R_{th} + R_L)^3}$$

$$\text{or,} \quad \frac{2 R_{th}}{R_L} + \frac{R_L}{R_L} = 2$$

$$\therefore R_{th} = R_L$$

Thus, the maximum power is

$$P_{max} = \left( \frac{V_{th}}{R_{th} + R_L} \right)^2 R_L = \left( \frac{V_{th}}{R_L + R_L} \right)^2 R_L = \frac{V_{th}^2}{4 R_L}$$

<Num. No. 60 : In numerical copy>