
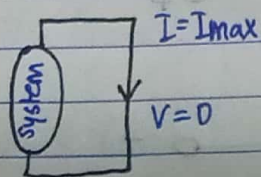


* Closed circuit

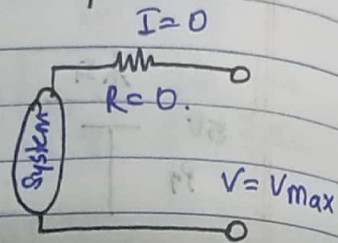

In closed circuit,
current is maximum
and no voltage if
unresistive.


* Open circuit



In open circuit,
current is zero
and the voltage
is maximum

<Num.No: 24/25/26/27/28/> ²⁹ In numerical copy.

Ladder Network

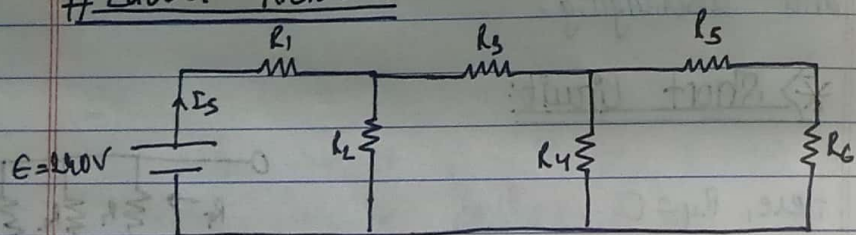


For this ladder network, we use
back to front to back approach.

Back to front to calculate total
resistance then move front to back to
find other unknown quantities.


Here, $R_1 = 5\Omega$ $R_2 = 6\Omega$ $R_3 = 4\Omega$
 $R_4 = 6\Omega$ $R_5 = 1\Omega$ $R_6 = 2\Omega$

Step 1: Redrawing the circuit,

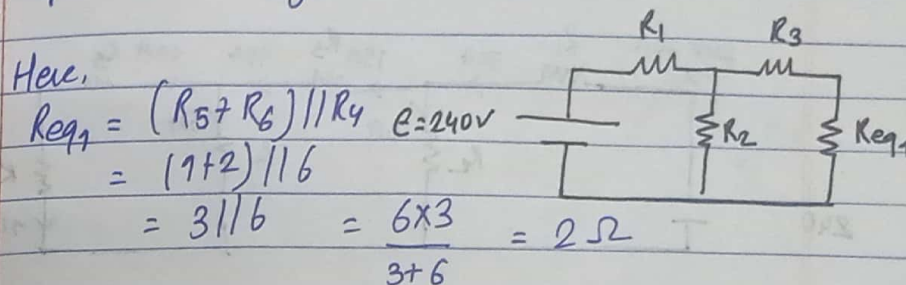

$\therefore Req_1 = 2\Omega$

Step 2: Redrawing the circuit,

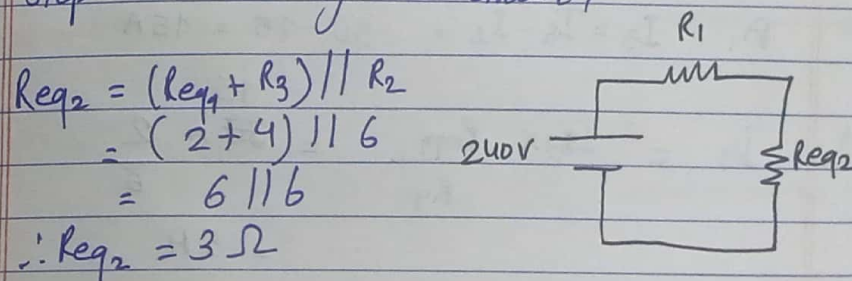

$\therefore Req_2 = 3\Omega$


Then,

$R_T = Req_2 + R_1 = 3 + 5 = 8\Omega$

So, $I_s = \frac{E}{R_T} = \frac{240}{8} = 30A$

Step 3: Show current division in original
circuit.

Then,

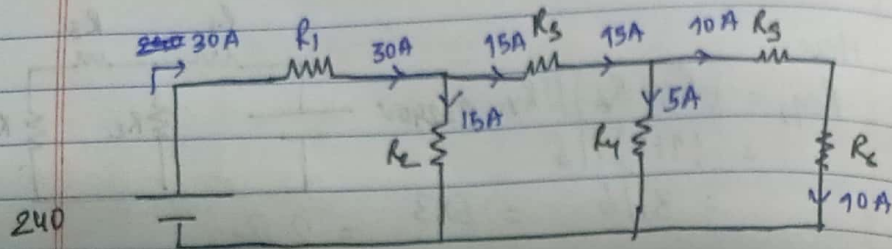

$$I_{R2} = I_s \times \frac{R_{eq2}}{(R_{eq1} + R_3)} = 30 \times \frac{3}{6}$$

$$\therefore I_2 = 15A$$

$$I_3 = I_s - I_2 = 30 - 15 = 15A$$

$$I_4 = I_{R3} \times \frac{R_{eq1}}{R_4} = 15 \times \frac{2}{6} = 5A$$

$$I_5 = I_3 - I_4$$


$$I_5 = 15 - 5$$

$$\therefore I_5 = 10A$$


$$V_6 = \frac{I_5 \times R_6}{R_1} = \frac{10 \times 2}{2} = 20V$$

Note: Circuit must be redrawn as we create equivalence of combination.


STAR-DELTA conversion:

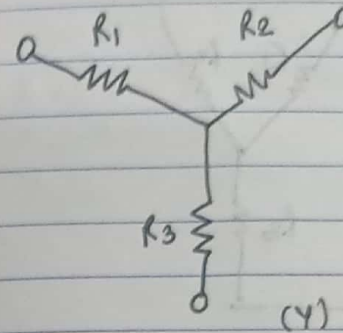


or,

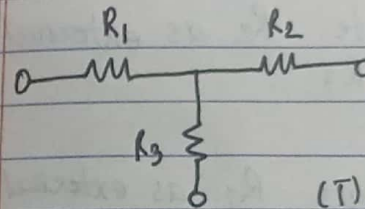

(T)

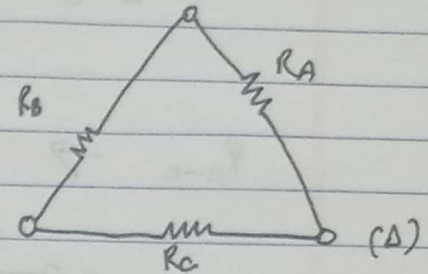


or,

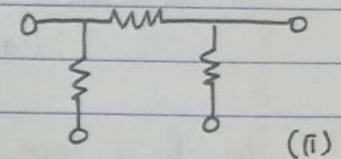


(Π)

Fig: Y(T) or Δ(Π) configuration.

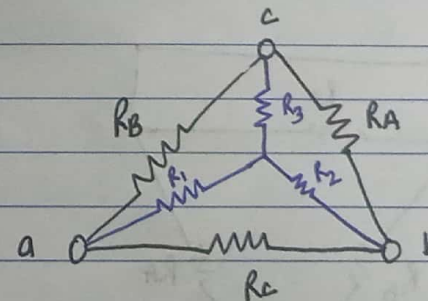To solve this kind of question, we convert Y to Δ or vice versa.




#Note: ∇

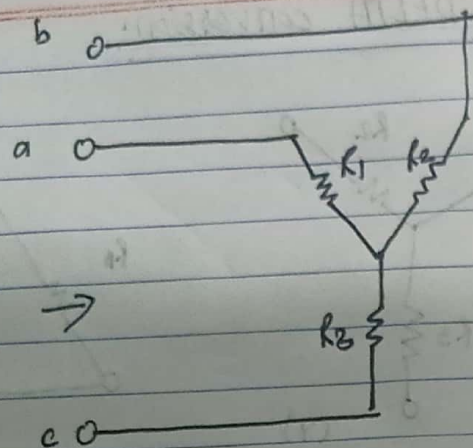

In R_{a-c} case, we eliminate R_2 as external path
 $\therefore R_{a-c} = R_1 + R_3$

In R_{b-c} case, we eliminate R_1 as external path
 $\therefore R_{b-c} = R_2 + R_3$

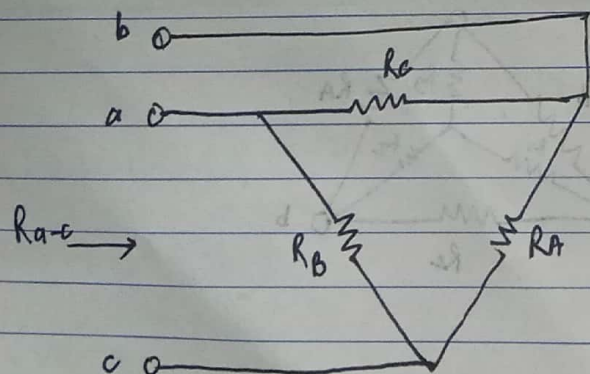In R_{a-b} case, we eliminate R_3 as external path
 $\therefore R_{a-b} = R_1 + R_2$



Here,

$$R_{AC} = R_B \parallel (R_A + R_C)$$

$$R_{BC} = R_A \parallel (R_B + R_C)$$

$$R_{AB} = R_C \parallel (R_A + R_B)$$

And,

$$R_{AC}(Y) = R_{AC}(\Delta)$$



$$R_{BC}(Y) = R_{BC}(\Delta)$$

$$R_{AB}(Y) = R_{AB}(\Delta)$$

Derivation:

To find expression for R_1, R_2, R_3 in terms of R_A, R_B, R_C and vice-versa.

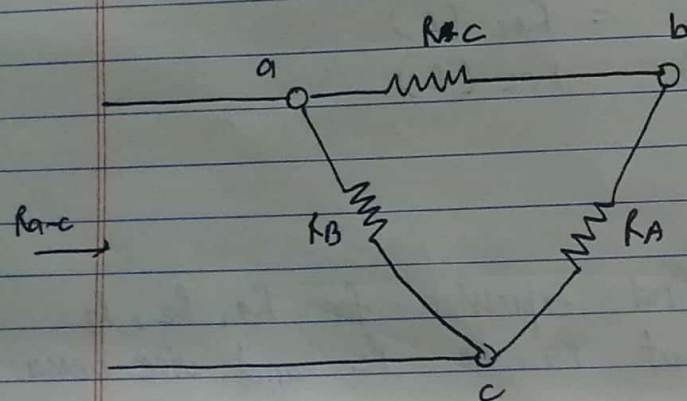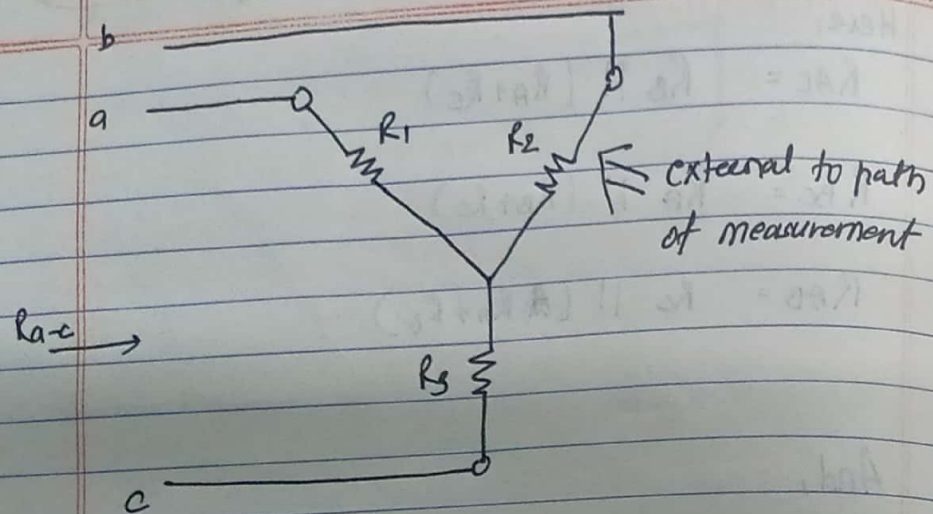The resistance between any two terminals of the Y-configuration will be the same with Δ -configuration inserted in place of the Y-configuration.



Let us convert the $\Delta(R_A, R_B, R_C)$ to $Y(R_1, R_2, R_3)$

We know,

$$R_{a-b}(Y) = R_{a-b}(\Delta)$$

so that,

$$R_1 + R_3 = \frac{R_B(R_A + R_C)}{R_B + (R_A + R_C)} \quad \text{--- (i)}$$

Using the same approach for a-b & b-c,

$$R_{a-b}(Y) = R_{a-b}(\Delta)$$

so that,

$$R_1 + R_2 = \frac{R_C(R_A + R_B)}{R_C + (R_A + R_B)} \quad \text{--- (ii)}$$

$$R_{b-c}(Y) = R_{b-c}(\Delta)$$

so that,

$$R_3 + R_2 = \frac{R_A(R_B + R_C)}{R_A + (R_B + R_C)} \quad \text{--- (iii)}$$

Subtracting eqⁿ (i) from (ii), we get

$$(R_1 + R_2) - (R_1 + R_3) = \left(\frac{R_C R_B + R_C R_A}{R_A + R_B + R_C} \right) - \left(\frac{R_B R_A + R_B R_C}{R_A + R_B + R_C} \right)$$

$$\text{or, } R_2 - R_3 = \frac{R_A R_C - R_B R_A}{R_A + R_B + R_C} \quad \text{--- (iv)}$$

Subtracting (iv) from (iii), we get.

$$(R_2 + R_3) - (R_2 - R_3) = \left(\frac{R_A R_B + R_A R_C}{R_A + R_B + R_C} \right) - \left(\frac{R_A R_C - R_B R_A}{R_A + R_B + R_C} \right)$$


$$\text{or, } 2R_3 = \frac{2R_A R_B}{R_A + R_B + R_C}$$

$$\therefore R_3 = \frac{R_A R_B}{R_A + R_B + R_C} \quad \text{--- (v)}$$

Similarly,

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C} \quad \text{--- (vi)}$$
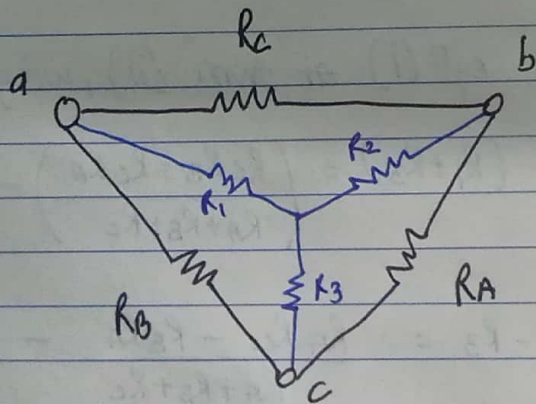
$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C} \quad \text{--- (vii)}$$



Note: Each resistor of the Y is equal to the product of the resistors in the two closest branches of Δ divided by the sum of total resistor in Δ .

For Y to Δ .

Dividing eqⁿ(v) by eqⁿ(vi).

$$\frac{R_3}{R_1} = \frac{(R_A R_B)}{(R_A + R_B + R_C)} \times \frac{(R_A + R_B + R_C)}{(R_B R_C)}$$

$$\therefore R_A = \frac{R_3 R_C}{R_1} \quad \text{--- (viii)}$$

Then,

Dividing eqⁿ(v) by eqⁿ(vii),

$$\frac{R_3}{R_2} = \frac{(R_A R_B)}{(R_A + R_B + R_C)} \times \frac{(R_A + R_B + R_C)}{(R_A R_C)}$$

$$\therefore R_B = \frac{R_3 R_C}{R_2} \quad \text{--- (ix)}$$

Substituting for R_A and R_B in eqⁿ(vii),

$$R_2 = \frac{\left(\frac{R_3 R_C}{R_1} \right) R_C}{\left(\frac{R_3 R_C}{R_2} \right) + \left(\frac{R_C R_3}{R_1} \right) + R_C}$$

$$= \frac{(R_3 R_2) / R_1}{(R_1 R_2 + R_1 R_3 + R_2 R_3) / R_1 R_2}$$

$$\text{or, } R_2 = \frac{R_3 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

$$\therefore R_2 = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3} \quad \text{--- (x)}$$

Similarly,

$$R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1} \quad R_B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

Note: The value of each resistor of the Δ is equal to the sum of the possible product combinations of the resistance of the Y divided by the resistance of the Y farthest from the resistor to be determined.

Special Case:

If $R_1 = R_2 = R_3 = R$ or $R_A = R_B = R_C = R$
then,

$$R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1} = \frac{3R^2}{R} = 3R$$

$$\therefore R_A = 3R = R_B = R_C.$$

$$\text{So, } R_{\Delta} = 3R_Y$$

< Num. No. 30/31/32 \Rightarrow In numerical copy >