

loops passing through in the same direction minus the assumed current through in the opposite direction.


b) The polarity of a voltage source is unaffected by the direction of the assigned loop currents.

→ Step 4: Solve the resulting simultaneous linear equations for the assumed loop currents.

< Num. No: 34 → In numerical | 35/36/37 → In numerical copy >

Supermesh:

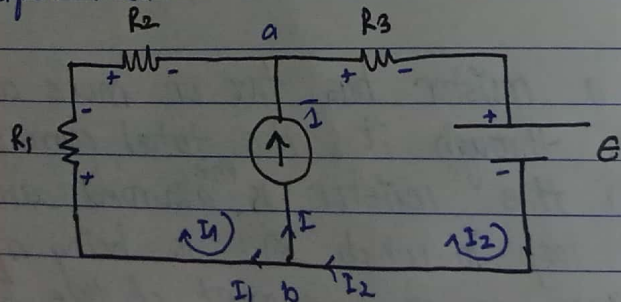If current source is between two-mesh systems, it is called a super-mesh.



For solving super-mesh system, the circuit is redrawn removing the current source.


At node b, applying KCL,

$$I_2 = I + I_1$$

$$\text{or } I = I_2 - I_1$$

$$\text{or } I = -I_1 + I_2 \quad \text{--- (i)}$$

Redrawing the circuit diagram, we get.

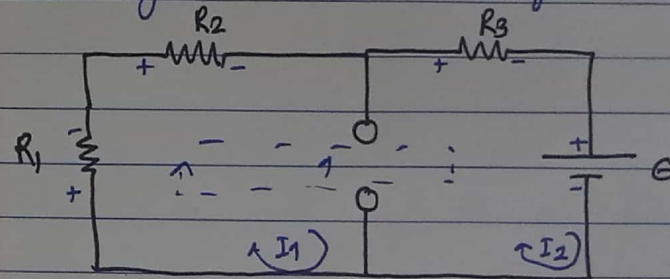

For loop 1,

$$-I_1 R_1 - I_2 R_2 - I_2 R_3 - E = 0$$

$$\therefore E + I_1 R_1 + I_2 R_2 + I_2 R_3 = 0$$

X) Three type of Q:

- i) Single current source at side
- ii) Middle of the two mesh.
- iii) Two or more supermesh.

< Num No: 38/39/40/41/42 → In numerical copy >

Nodal Analysis

Nodal analysis is a method that is used to solve planar circuits for any currents at any place in electrical circuits using KCL.

Steps to solve:

- Step 1: Firstly, we calculate how many nodes there are in our circuits. If there are 'n' nodes, there are n-1 equations.
- Step 2: We take a reference node which is mostly grounded. Generally, the most common node is grounded. It is referred as zero (0) node.
- Step 3: At every node, we apply KCL. If we are not supplied with current, we assume the current is travelling out from the node.

We solve the obtained equations to find voltage.


< Num.No: 43, 44, 45: In numericals copy >

Super-node:

A super-node exists when an ideal voltage source appears between any two nodes of an electric circuit.

To solve super-mesh:

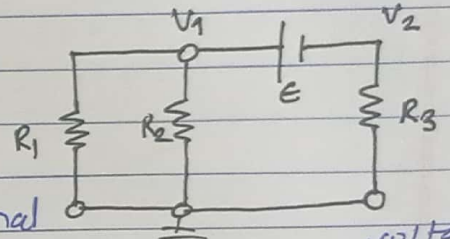- First, we write the equation for the voltage.




The positive terminal difference with negative terminal difference gives the super-node voltage. Here,

$$V_1 - V_2 = E.$$

- Now, the voltage is replaced with a short circuit and then we find equations using previous notation. We solve both nodes in one eqⁿ.

$$I_1 + I_2 + I_3 = 0$$
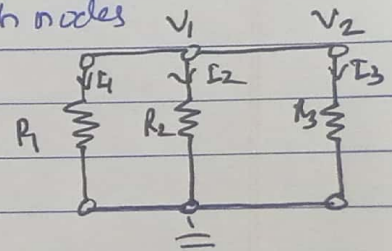
$$\text{or } \frac{V_1}{R_1} + \frac{V_1}{R_2} + \frac{V_2}{R_3} = 0.$$



*) Note

< Num.No. 46, 47, 48 = In numericals copy >

(X) Note: (Note copy content)

When to use mesh analysis or node analysis

(i): If number of nodes = number of mesh, we can use any method

(ii) If number of nodes less than number of mesh, we use nodal analysis.

(iii) If number of nodes less than number of mesh, we use mesh analysis.