

Here,

$$R_{a-c} = \frac{(g+1)}{(g+1)} (g \parallel R_1) + (g+R_3)$$


[∵  $R_2$  is external path]

$$= \frac{g \times 2}{g+2} + \frac{g \times 2}{g+2}$$

$$= \frac{36}{11}$$

$$\therefore R_{a-c} = R_T = 3.27 \Omega$$

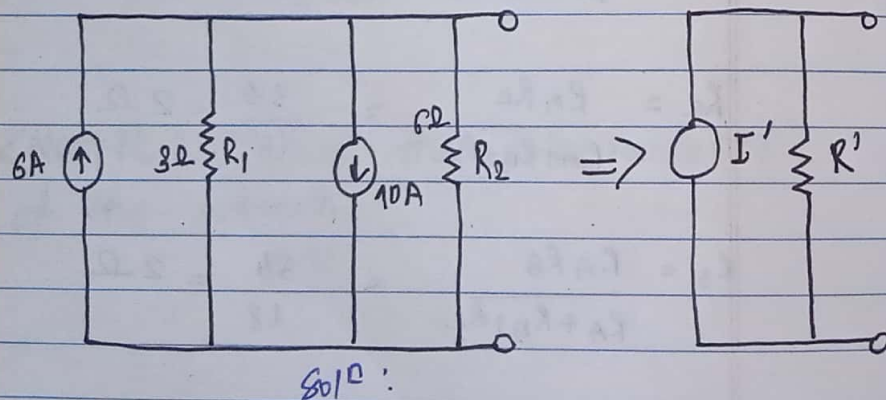
<Num. No. 33>: Convert the parallel current source to a single current source.




$$\therefore I' = 10 - 6 = 4A \text{ (↓)}$$

$$\therefore R' = \frac{R_1 R_2}{R_1 + R_2} = \frac{6 \times 3}{6 + 3} = 2 \Omega$$

Then,

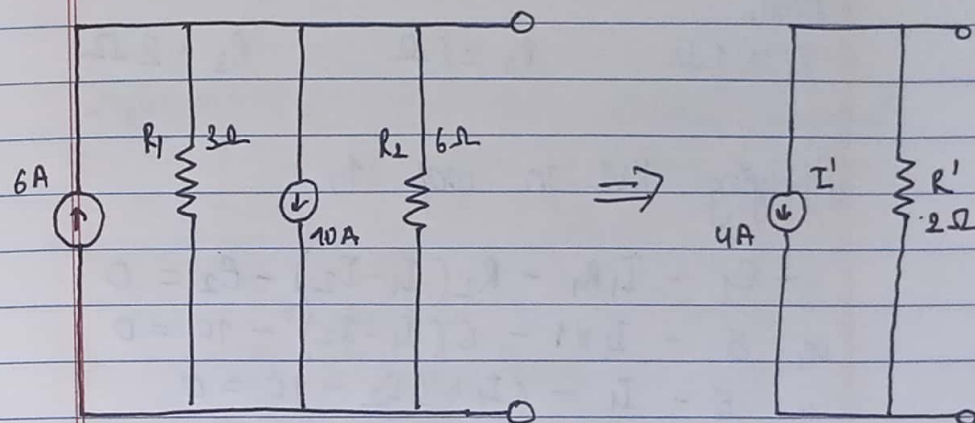
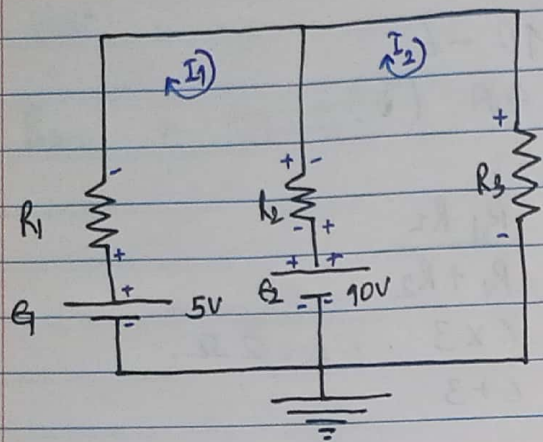
<Num. No. 34>: Find the current through each branch of the network in figure.



Given,

$$R_1 = 1 \Omega$$

$$R_2 = 6 \Omega$$

$$R_3 = 2 \Omega$$

Applying KVL in loop 1,

$$+E_1 - I_1 R_1 - R_2(I_1 - I_2) - E_2 = 0$$

$$\text{or, } 5 - I_1 \times 1 - 6(I_1 - I_2) - 10 = 0$$

$$\text{or, } 5 - I_1 - 6I_1 + 6I_2 - 10 = 0$$

$$\text{or, } -7I_1 + 6I_2 = 5 \quad \text{--- (i)}$$

Applying KVL in loop 2,

$$+E_2 - R_2(I_2 - I_1) - R_3 I_2 = 0$$

$$\text{or, } 10 - 6(I_2 - I_1) - 2I_2 = 0$$

$$\text{or, } 3I_1 - 4I_2 = -5 \quad \text{--- (ii)}$$

Solving (i) and (ii), we get.

$$I_1 = 1 \text{ A}$$

$$I_2 = 2 \text{ A}$$

Now,


$$I_{R1} = 1 \text{ A } (\uparrow)$$

$$I_{R3} = 2 \text{ A } (\downarrow)$$

$$I_{R2} = I_2 - I_1 = 1 \text{ A } (\uparrow) \text{ for } I_2 \}$$

<Num.No.35>: Find the branch current.

Soln:

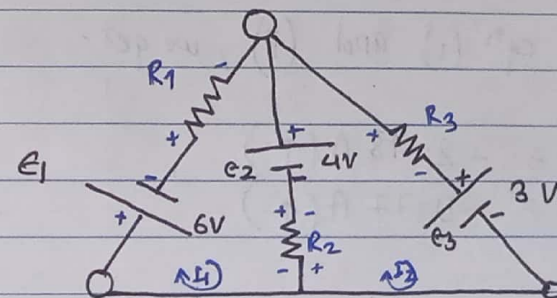

Given,

$$R_1 = 2 \Omega$$

$$R_2 = 4 \Omega$$

$$R_3 = 6 \Omega$$



Applying KVL in loop 1,

$$-E_1 - I_1 R_1 - E_2 - R_2(I_1 - I_2) = 0$$

$$\text{or, } -6 - 2I_1 - 4 - 4(I_1 - I_2) = 0$$

$$\text{or, } -6 - 2I_1 - 4 - 4I_1 + 4I_2 = 0$$

$$\text{or, } -6I_1 + 4I_2 = 10 \quad \text{--- (i)}$$

Applying KVL in loop 2,

$$-E_3 - R_2(I_2 - I_1) + E_2 - R_3 I_2 = 0$$

$$\text{or, } -3 - 4I_2 + 4I_1 + 4 - 6I_2 = 0$$

$$\text{or, } 4I_1 - 10I_2 = -1 \quad \text{--- (ii)}$$

Solving eq<sup>n</sup> (i) and (ii), we get.

$$\therefore I_1 = -2.18 \text{ A } (\uparrow)$$

$$\therefore I_2 = -0.77 \text{ A } (\uparrow)$$


Now,

$$IR_1 = -2.18 \text{ A } (\uparrow)$$

$$IR_3 = -0.77 \text{ A } (\downarrow)$$

$$IR_2 = I_1 - I_2 = -1.41 \text{ A } (\downarrow) \text{ for } I_1$$
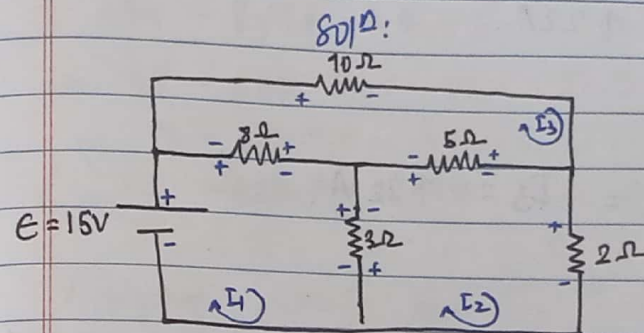
<Num. No. 36>: Find the current through the  $10\Omega$  resistor of the network.



Applying KVL at loop 1,

$$+E_1 - 8(I_1 - I_3) - 3(I_1 - I_2) = 0$$

$$\text{or, } 15 - 8I_1 + 8I_3 - 3I_1 + 3I_2 = 0$$

$$\text{or, } -11I_1 + 3I_2 + 8I_3 = -15 \quad \text{--- (i)}$$

Applying KVL at loop 2,

$$-2I_2 - 3(I_2 - I_1) - 5(I_2 - I_3) = 0$$

$$\text{or, } -2I_2 - 3I_2 + 3I_1 - 5I_2 + 5I_3 = 0$$

$$\text{or, } 3I_1 - 10I_2 + 5I_3 = 0 \quad \text{--- (ii)}$$

Applying KVL at loop 3,

$$-5(I_3 - I_2) - 8(I_3 - I_1) - 10I_3 = 0$$

$$\text{or, } -5I_3 + 5I_2 - 8I_3 + 8I_1 - 10I_3 = 0$$

$$\text{or, } 8I_1 + 5I_2 - 23I_3 = 0 \quad \text{--- (iii)}$$

Solving (i), (ii), (iii),

$$I_1 = 2.63 \text{ A}$$

$$I_2 = 1.39 \text{ A}$$


$$I_3 = 1.22 \text{ A}$$

Now,

$$\therefore I_{R10} = I_3 = 1.22 \text{ A}$$

(Num. No 37): Find all the branch current.

Soln:

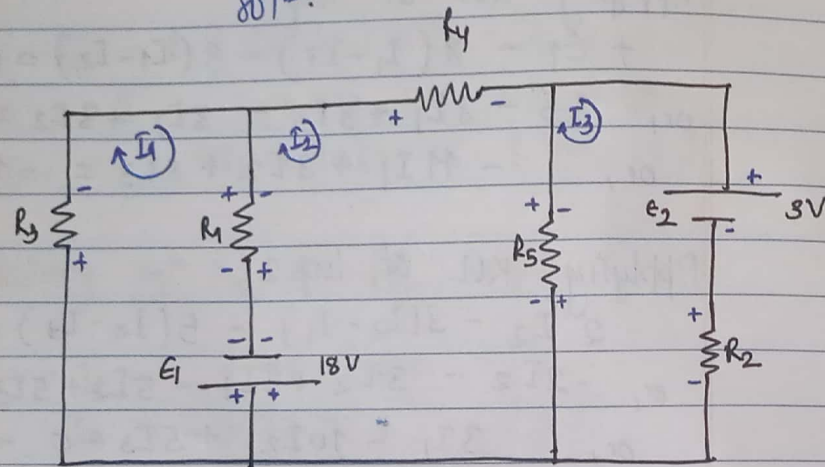

Given,

$$R_1 = 7.5 \text{ k}\Omega$$

$$R_2 = 3.3 \text{ k}\Omega$$

$$R_3 = 6.8 \text{ k}\Omega$$

$$R_4 = 7.5 \text{ k}\Omega$$

$$R_5 = 2.2 \text{ k}\Omega$$

Applying KVL in loop 1,

$$+E_1 - R_3 I_1 - R_1 (I_1 - I_2) = 0$$

$$\text{or, } 18 - 6800 I_1 - 7500 (I_1 - I_2) = 0$$

$$\text{or, } 18 - 6800 I_1 - 7500 I_1 + 7500 I_2 = 0$$

$$\text{or, } -14300 I_1 + 7500 I_2 = -18 \quad \text{--- (i)}$$

Applying KVL in loop 2,

$$-E_1 - R_1 (I_2 - I_1) - R_4 I_2 - R_5 (I_2 - I_3) = 0$$

$$\text{or, } -18 - 7500 (I_2 - I_1) - 7500 I_2 - 2200 (I_2 - I_3) = 0$$

$$\text{or, } -18 - 7500 I_2 + 7500 I_1 - 7500 I_2 - 2200 I_2 + 2200 I_3 = 0$$

$$\text{or, } 7500 I_1 - 17200 I_2 + 2200 I_3 = 18 \quad \text{--- (ii)}$$

Applying KVL in loop 3,

$$-E_2 - 3300 I_3 - 2200 (I_3 - I_2) = 0$$

$$\text{or, } -3 - 3300 I_3 - 2200 I_3 + 2200 I_2 = 0$$

$$\text{or, } 2200 I_2 - 5500 I_3 = 3 \quad \text{--- (iii)}$$

Solving (i), (ii) and (iii),

$$I_1 = 9.85 \times 10^{-4} = 0.985 \text{ mA}$$

$$I_2 = -5.20 \times 10^{-4} = -0.520 \text{ mA}$$

$$I_3 = 7.535 \times 10^{-4} = 0.753 \text{ mA}$$



Now,

$$I_{R3} = I_1 = 0.985 \text{ mA} \quad (\uparrow)$$

$$I_{R1} = I_1 - I_2 = 0.580 + 0.520 = 1.5 \text{ mA} \quad (\downarrow)$$

$$I_{R4} = I_2 = -0.520 \text{ mA} \quad (\rightarrow)$$

$$I_{R5} = I_2 - I_3 = -0.520 + 0.753 = 0.233 \text{ mA} \quad (\downarrow)$$

$$I_{R2} = I_3 = 0.753 \text{ mA} \quad (\downarrow)$$