

<Num.No.23>: Find the R_T , I_T , I_1 , I_2 and I_3 using CDR.
 Soln.


Given,

$$\text{Voltage (V)} = 64 \text{ V}$$

$$R_1 = 5 \text{ k}\Omega$$

$$R_2 = 6 \text{ k}\Omega$$

$$R_3 = 8 \text{ k}\Omega$$

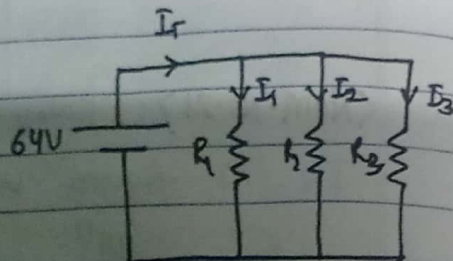

(i) Let ' R_T ' be the total resistance.

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\text{or, } \frac{1}{R_T} = \frac{1}{5000} + \frac{1}{6000} + \frac{1}{8000}$$

$$\text{or, } \frac{1}{R_T} = 4.916 \times 10^{-7}$$

$$\therefore R_T = 2033.89 \Omega$$

$$(ii) I_T = \frac{V}{R_T} = \frac{64}{2033.89} = 0.03146 \text{ A} = 31.46 \text{ mA}$$

$$(iii): I_1 = I_T \times \frac{R_T}{R_1} = \frac{31.46 \times 2033.89}{5000} = 12.79 \text{ mA}$$

$$I_2 = I_T \times \frac{R_T}{R_2} = \frac{31.46 \times 2033.89}{6000} = 10.66 \text{ mA}$$

$$I_3 = 31.46 - 12.79 - 10.66$$

$$\therefore I_3 = 7.99 \text{ mA}$$

<Num.No.24>: Find the current I_3 for the series parallel network in figure.
 Soln:


Here,

$$R_1 = 2 \text{ k}\Omega$$

$$R_2 = 12 \text{ k}\Omega$$

$$R_3 = 6 \text{ k}\Omega$$


$$V = 54 \text{ V}$$

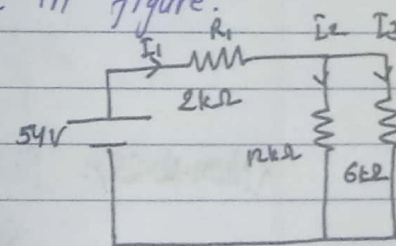

Now,

$$R' = R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3} = \frac{12 \times 6}{12 + 6} = 4 \text{ k}\Omega$$

So, rewriting the circuit,

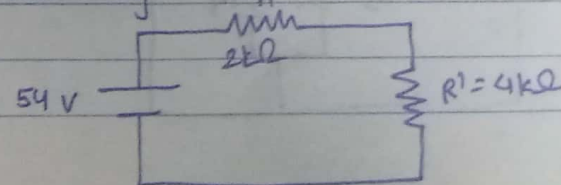

So, $R_T = R_1 + R' = 2 + 4 = 6 \text{ k}\Omega$

(i): $I_T = \frac{V}{R_T} = \frac{54}{6} = 9 \text{ mA}$

~~$I_1 = I_T \times \frac{R_T}{R_1} = \frac{9 \text{ mA} \times 6}{2}$~~


$I_2 = I_T \times \frac{R_T}{R_2} = \frac{9 \text{ mA} \times 6}{12} = 3 \text{ mA}$

$\therefore I_4 = I_3 + I_2$

or, $I_2 = 9 \text{ mA} - 3 \text{ mA} = 6 \text{ mA}$

<Num. No. 25>: Determine I_4 , I_1 , I_3 and V_2 .

Soln:

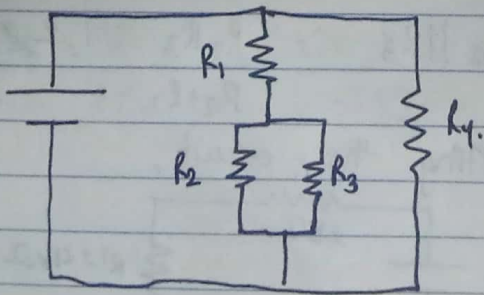

Here,

$R_1 = 6.8 \text{ k}\Omega$

$R_2 = 18 \text{ k}\Omega$

$R_3 = 2 \text{ k}\Omega$

$R_4 = 8.2 \text{ k}\Omega$


$V = 12 \text{ V}$

Now,

(i): $R' = \frac{R_3 R_4}{R_3 + R_4} = \frac{2 \times 8.2}{2 + 8.2} = 1.8 \text{ k}\Omega$

(ii): $R'' = R_1 + R' = 1.8 + 6.8 \text{ k}\Omega = 8.6 \text{ k}\Omega$

Rewriting circuit,

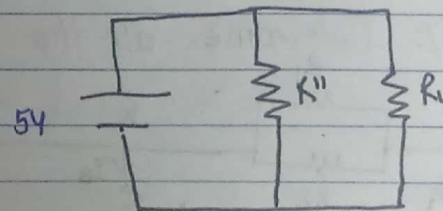

$R_T = \frac{R'' R_4}{R'' + R_4} = \frac{8.6 \times 8.2}{8.6 + 8.2} = 4.2 \text{ k}\Omega$

So, $I_T = \frac{V}{R_T} = \frac{54}{4.2} = 2.85 \text{ mA}$


$$(i): I_4 = I_T \times \frac{R_T}{R_4} = \frac{2.85 \times 4.2}{8.2} = 1.46 \text{ mA}$$

$$(ii): I_1 = I_T \times \frac{R_T}{R_1} = \frac{2.85 \times 4.2}{6.8}$$

$$I_T - I_4 = 1.39 \text{ mA}$$

$$(iii): V_2 = V \times \frac{R'}{R''} = \frac{12 \times 1.8}{8.6} = 2.51 \text{ V}$$
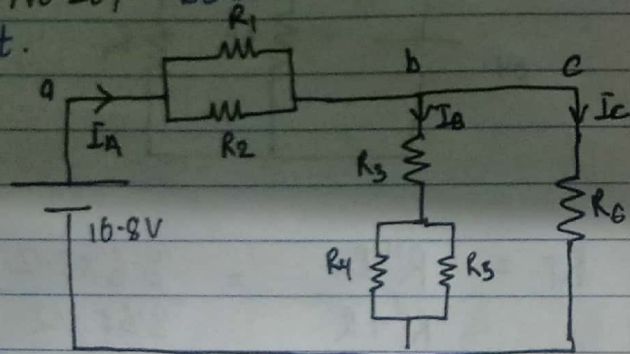
<Num. No. 26>: Determine all the unknown current.



Solⁿ: Here,

$$R_1 = 9 \Omega$$

$$R_3 = 4 \Omega$$


$$R_5 = 3 \Omega$$

$$R_2 = 6 \Omega$$

$$R_4 = 6 \Omega$$

$$R_6 = 3 \Omega$$

Rewriting the circuit,

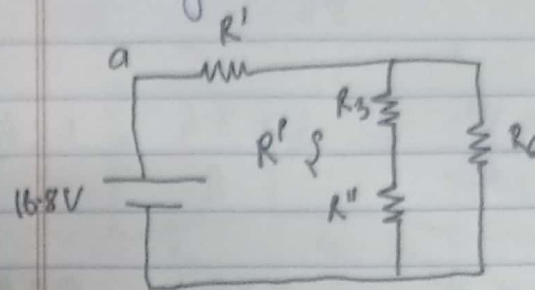

$$R' = \frac{9 \times 6}{9 + 6} = 3.6 \Omega$$

$$R'' = \frac{6 \times 3}{6 + 3} = 2 \Omega$$

$$R' = R_3 + R'' = 6 \Omega$$

$$R''' = R'' \parallel R_6 = \frac{R'' R_6}{R'' + R_6} = \frac{6 \times 3}{9} = 2 \Omega$$

$$\text{So, } R_T = 3.6 + 2 = 5.6 \Omega$$

Now,

$$i) I_A = \frac{V}{R_T} = \frac{16.8}{5.6} = 3A$$

$$ii) I_1 = I_T \times \frac{R'}{R_1} = 3 \times \frac{3.6}{9} = 1.2A$$

$$iii) I_2 = I_T \times \frac{R'}{R_2} = 3 \times \frac{3.6}{6} = 1.8A$$

We know,

$$V_b = 3 \times 3.6 = 10.8V$$


$$V_{ab} = V_a - V_b = 16.8 - 10.8 = 6V$$

Since b and c are in parallel,

$$I_B = \frac{V_{ab}}{R'} = \frac{6}{6} = 1A$$

$$I_c = \frac{V_c}{R_6} = \frac{6}{3} = 2A$$
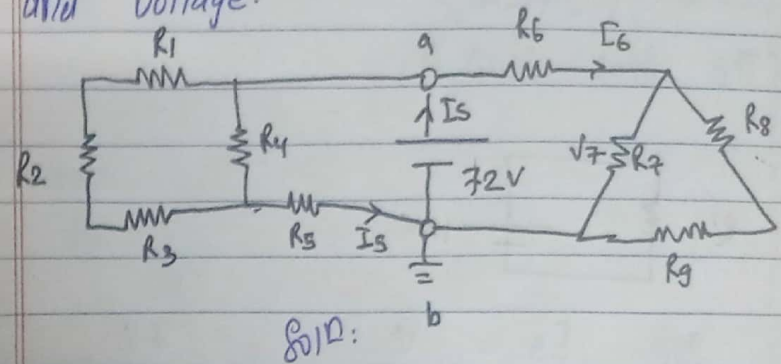
<Num. No. 27>: Calculate the indicated current and voltage.



Soln:

Given,

$$R_1 = 4k\Omega$$

$$R_4 = 24k\Omega$$

$$R_7 = 9k\Omega$$

$$R_2 = 8k\Omega$$

$$R_5 = 12k\Omega$$

$$R_8 = 3k\Omega$$



$$V = 72V$$

$$R_3 = 12k\Omega$$

$$R_6 = 12k\Omega$$

$$R_9 = 6k\Omega$$

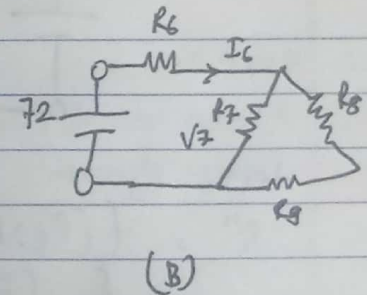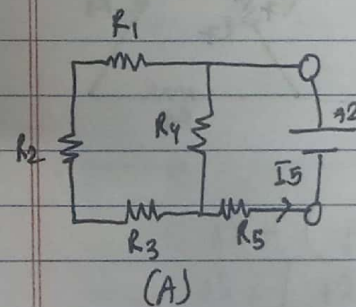Let us divide the circuit into two parts:




Taking circuit A,

$$R' = ((R_1 + R_2 + R_3) \parallel R_4) + R_5$$

$$= \left(\frac{(R_1 + R_2 + R_3) \times R_4}{R_1 + R_2 + R_3 + R_4} \right) + R_5$$

$$= \left(\frac{24 \times 24}{24 + 24} \right) + 12 = 24 \text{ k}\Omega$$


The final circuit A,

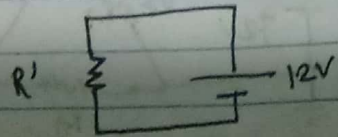

$$\text{So, } I_5 = \frac{V}{R'} = \frac{72}{24}$$

$$\therefore I_5 = 3 \text{ mA}$$

Taking circuit B,

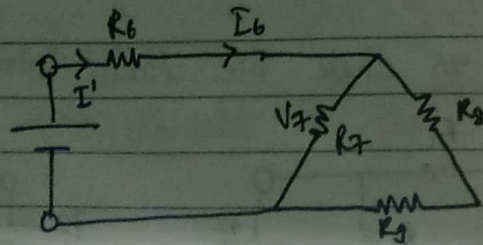


Here,

$$\begin{aligned} R'' &= ((R_8 + R_9) \parallel R_7) + R_6 \\ &= \left[\frac{(R_8 + R_9) \times R_7}{R_8 + R_9 + R_7} \right] + R_6 \\ &= \left[\frac{(3 + 6) \times 9}{3 + 6 + 9} \right] + 12 \end{aligned}$$

$$\therefore R'' = 16.5 \text{ k}\Omega$$

Rewriting circuit B,

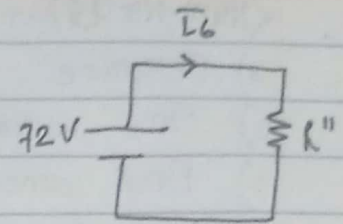

Now,

$$R_T \quad \frac{1}{R_T} = \frac{1}{R'} + \frac{1}{R''}$$

$$\text{or } \frac{1}{R_T} = \frac{24 + 16.5}{24 \times 16.5} \quad \therefore R_T = 9.77 \Omega$$

$$I_5 = \frac{V}{R_T} = \frac{72}{9.77} = 7.35 \text{ mA}$$

So,

$$\begin{aligned} I' &= I_5 - I_5 \\ &= 7.35 - 3 = 4.35 \text{ mA} = I_6 \end{aligned}$$

[\therefore same current flows through series resistor]

from KCL, at a,

I

Now,


$$\begin{aligned} V_6 &= I_6 R_6 \\ &= \cancel{5.22 \text{ V}} 52.2 \text{ V} \end{aligned}$$

$$\therefore V_7 = 72 - 52.2 = 19.8 \text{ V}$$

<Num-No-28>: For the network in figure,

- Determine V_a , V_b , V_c .
- Find voltage V_{ac} & V_{bc}
- Find current I_2
- Find the source current I_{s3} .

Solⁿ:

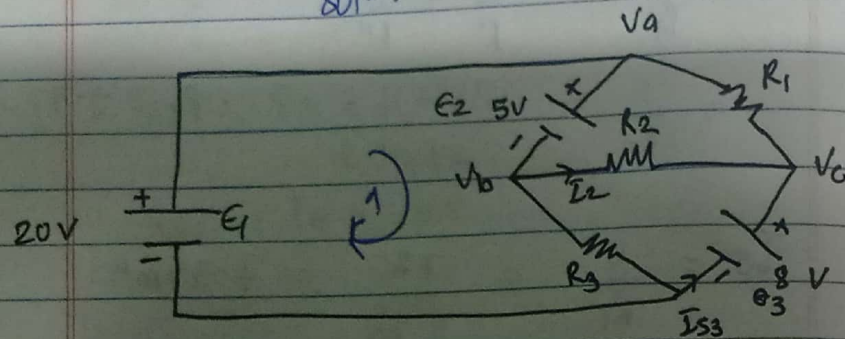

Given,

$$R_1 = 10 \Omega$$

$$R_2 = 4 \Omega$$

$$R_3 = 5 \Omega$$

a):

- $V_a = 20 \text{ V}$ [Voltage directly across E_1]
- $V_{bc} = 8 \text{ V}$ [Voltage directly across E_3]

Applying KVL in loop 1,
 $+E_1 - E_2 - V_3 = 0$

Hence, $V_3 = \text{voltage across } R_3 = V_b$

So,

$$V_b = 20 - 5 = 15 \text{ V}$$

b): Using double subscript method,


$$V_{ac} = V_a - V_c = 20 - 5 = 15 \text{ V}$$

$$V_{bc} = V_b - V_c = 15 - 8 = 7 \text{ V}$$

$$c): I_2 = \frac{V_2}{R_2}$$

$$= \frac{V_{bc}}{R_2} = \frac{7}{4} = 1.75 \text{ A}$$

Redrawing the circuit,

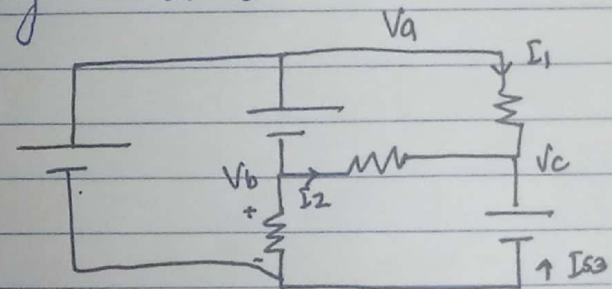

Applying KCL at node C,

$$\sum I_{in} = \sum I_{out}$$

$$I_1 + I_2 + I_3 = 0$$

$$\therefore I_{s3} = -I_1 - I_2$$

$$= -\frac{V_1}{R_1} - I_2 = -\frac{V_{ac}}{R_1} - I_2$$

$$= -\frac{15}{10} - 1.75 = -1.5 - 1.75 = -3.25 \text{ A}$$