

### # Superposition Theorem:

The current or voltage through or across any element of a network is equal to the algebraic sum of the currents or voltages produced independently by each source.

\* When removing a voltage source from a network schematic, we replace it with a direct connection (short circuit) of zero ohm ( $0\Omega$ ). Any internal resistance associated with the source must remain in the network.

\* When removing a voltage source from a network schematic, replace it with an open circuit of infinite ( $\infty$ )  $\Omega$ .

Since the effect of each source will be determined independently, the number of networks to be analyzed will equal the number of sources.

Mathematically,

$$I = I' + I'' + \dots$$

$$V = V' + V'' + \dots$$

→ This theorem is used in linear circuits.

< Num. No. 48/49/50 ⇒ In numericals only >

### # Thevenin's Theorem:

Any two terminals DC network can be replaced by an equivalent circuit consisting solely of a voltage source and series resistor as shown in figure.

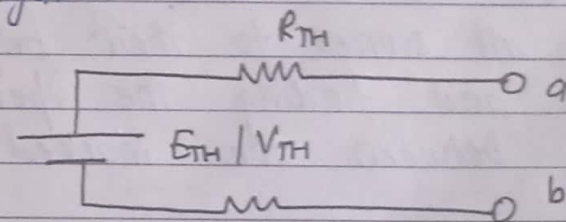


Fig. Thevenin's Equivalent Circuit.

Date \_\_\_\_\_  
Page \_\_\_\_\_

### (\*) Procedure:

(i) Remove that portion of the network <sup>except</sup> where the Thevenin's Equivalent Circuit is found.

(ii) Mark the terminal of the remaining two terminal network.

(iii):  $R_{TH}$ :

Calculate the  $R_{TH}$  by first setting all sources to zero and then finding the equivalent resistance between two marked terminals.

(iv):  $V_{TH}$ :

Calculate the  $V_{TH}$  from by first resulting all sources to their original position and finding the open-circuit voltage between the marked terminals.

(v): Conclusion:

Draw the Thevenin's Equivalent circuit with the position of the circuit previously removed replaced


Date \_\_\_\_\_  
Page \_\_\_\_\_

between the two terminals of equivalent circuit.

(X): Note:


$$(i) \quad I_{R1} = \frac{I \times R_2}{(R_1 + R_2)}$$
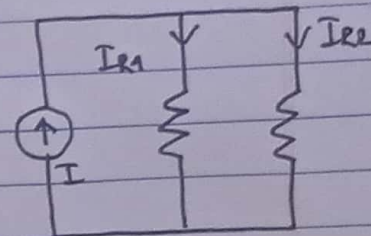
$$I_{R2} = \frac{I \times R_1}{(R_1 + R_2)}$$



$$(ii) \quad V_1 = \frac{V \times R_1}{(R_1 + R_2)}$$
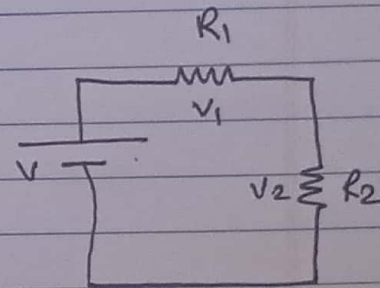
$$V_2 = \frac{V \times R_2}{(R_1 + R_2)}$$



< Num. No 51/52  $\Rightarrow$  In numerical copy >.