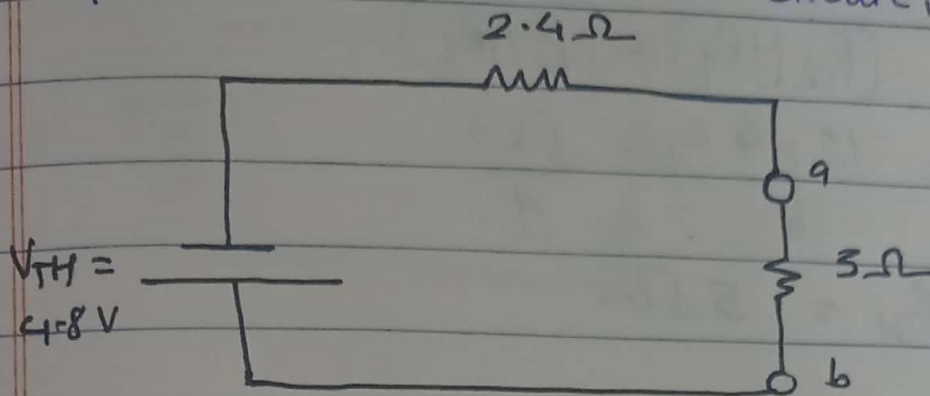


Using



Step: 5: V_{TH} and R_{TH} , drawing the equivalent Thevenin's circuit,



<Num. No. 53>: Find the Thevenin's equivalent circuit for the networks between point a and b.

Soln.

Step 1, 2

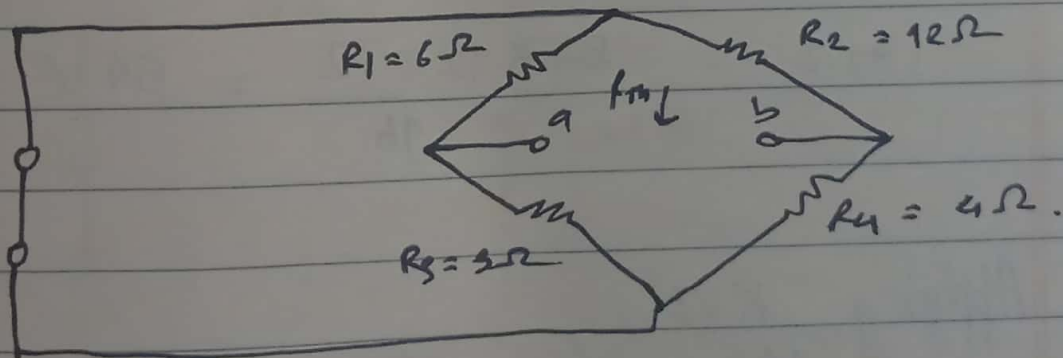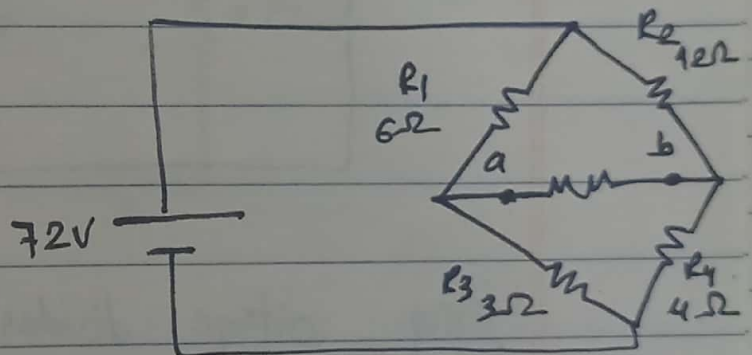


Now,

$$R_{TH} = (R_2 || R_4) + (R_1 || R_3)$$

$$= \frac{12 \times 4}{16} + \frac{6 \times 3}{9}$$

$$\therefore R_{TH} = 5 \Omega$$

Again,

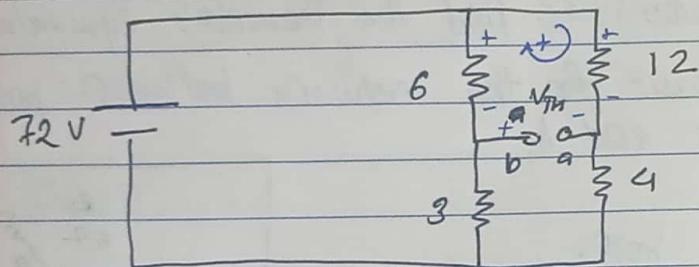

Using voltage divider rule,

$$V_{6\Omega} = \frac{72 \times 6}{9} = 48 \text{ V}$$


$$V_{12\Omega} = \frac{54 \times 12}{16} = 54 \text{ V}$$

Applying KVL,


$$V_{TH} + V_{6\Omega} - V_{12\Omega} = 0$$

$$\therefore V_{TH} = 6 \text{ V}$$

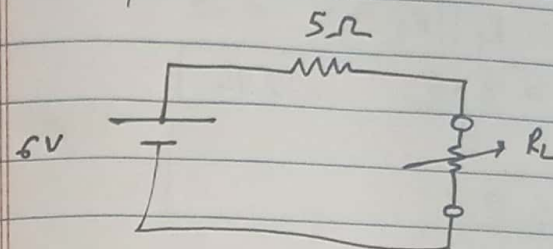The equivalent ~~circuit~~ ^{Thermin's} circuit is




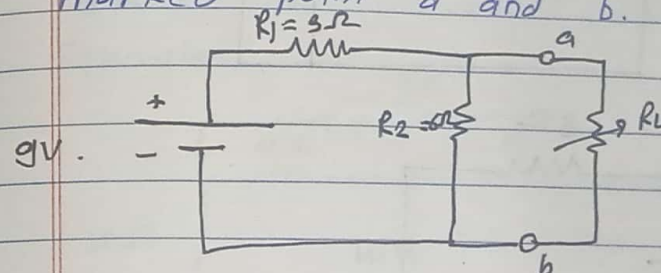(Num. No 54): Find the Norton's equivalent circuit for the network between marked point a and b.



Solⁿ:

Step 1, 2:

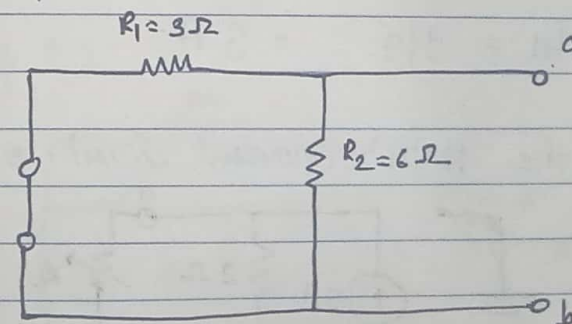


Now

$$R_N = R_1 \parallel R_2$$


$$= \frac{3 \times 6}{9} = 2 \Omega$$

$$\therefore R_N = 2 \Omega$$

Step: 3:

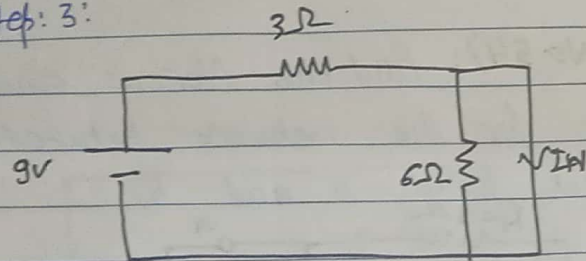


Then,

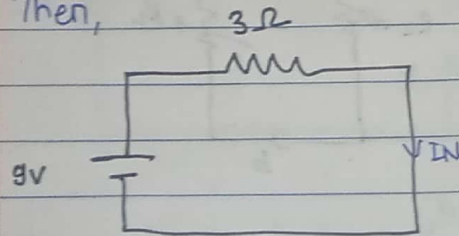


$$I_N = 9/3 = 3 \text{ A}$$


So the Norton's equivalent circuit is

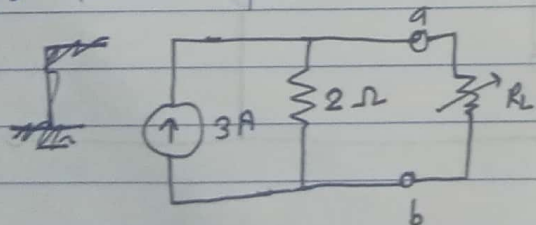


The equivalent Thevenin's circuit is,

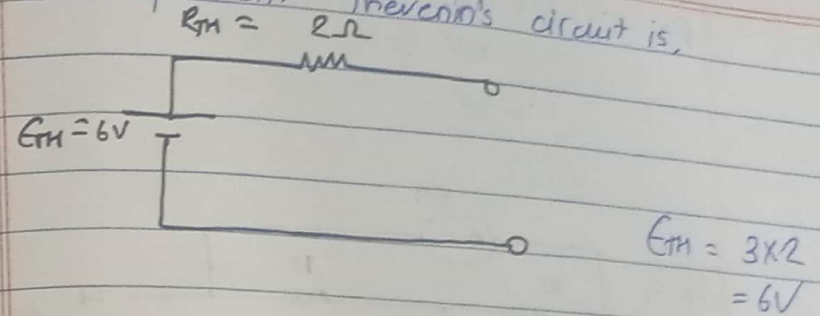

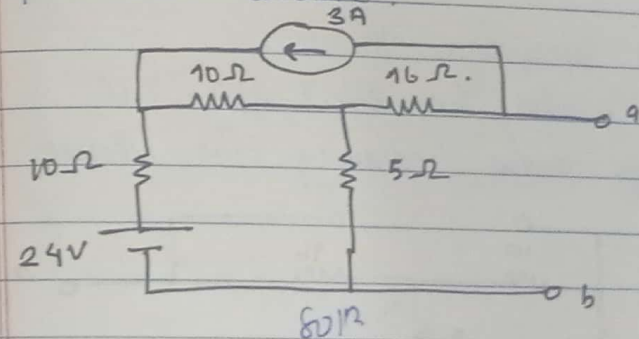(Num. No. 55): Obtained the Thevenin's equivalent of terminal a-b of the circuit and convert it into Norton's equivalent circuit.




Step 1, 2:

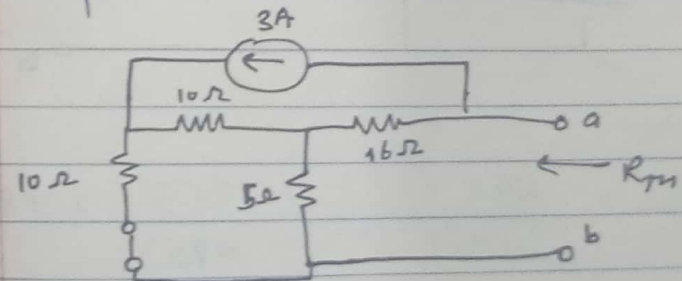

$$R_{TH} = \left\{ (10+10) \parallel 5 \right\} + 16$$


$$= \frac{4 \times 20 \times 5}{25} + 16$$

$$= 20 \Omega$$

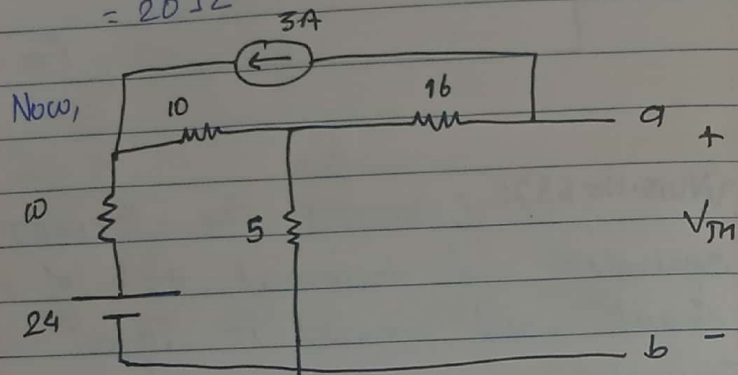

Using superposition theorem,

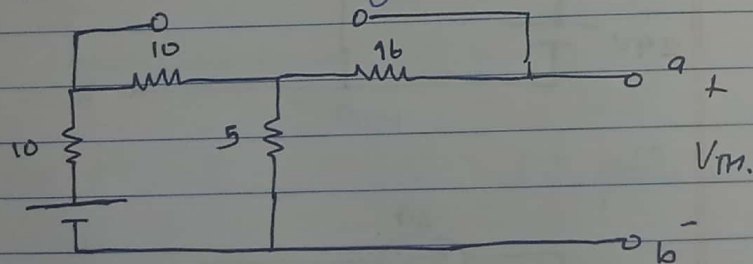
Consider the effect of 24V voltage source, redrawing the circuit,



Now,

$$V_{5\Omega} = \frac{24 \times 5}{(10+10 \parallel 5)} = \frac{24 \times 5}{25} = 4.8 \text{ V}$$

Redrawing the circuit,

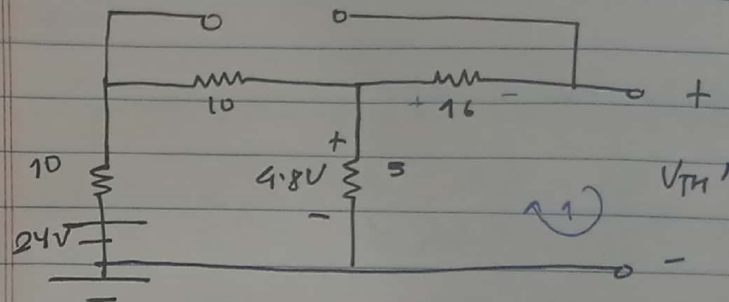


In loop 1,

$$V_5 - V_{16} - V_{TH}'$$

$$\therefore V_{TH}' = -4.8 \text{ V}$$

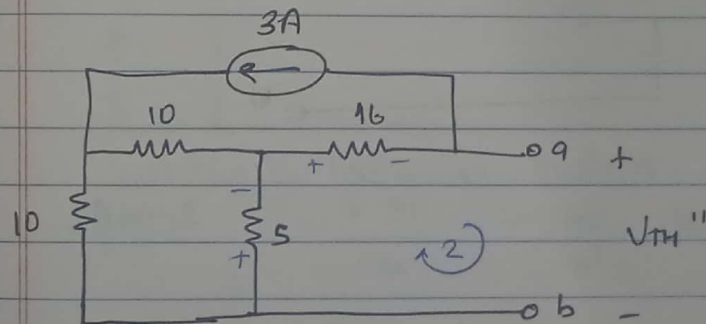Considering the effect of 3A current, redrawing the circuit,



Now, using current divider rule,

$$I_{5\Omega} = \frac{10 \times 3}{25} = 1.2 \text{ A}$$

$$\therefore V_{5\Omega} = 5 \times 1.2 = 6 \text{ V}$$

And $V_{6\Omega} = I \times R_{6\Omega}$
 $= 48 \text{ V}$

Applying KVL in loop ^


$$-V_{5\Omega} - V_{6\Omega} - V_{TH}'' = 0$$

$$\therefore V_{TH}'' = -54 \text{ V}$$

Now,


$$V_{TH} = V_{TH}' + V_{TH}'' = 4.8 - 54 = -49.2 \text{ V}$$

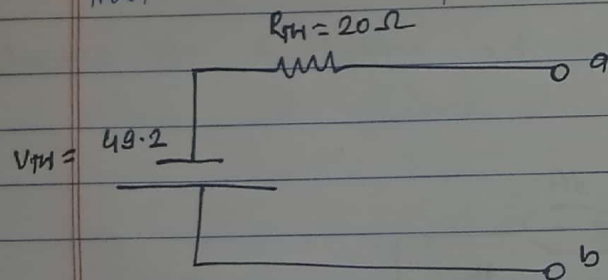Thus, the thevenin's equivalent circuit is,




The Norton's equivalent circuit is,

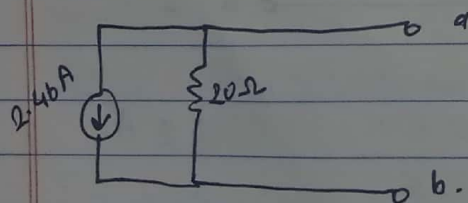
$$I_N = \frac{V_{TH}}{R_{TH}} = \frac{49.2}{20} = 2.46 \text{ A}$$


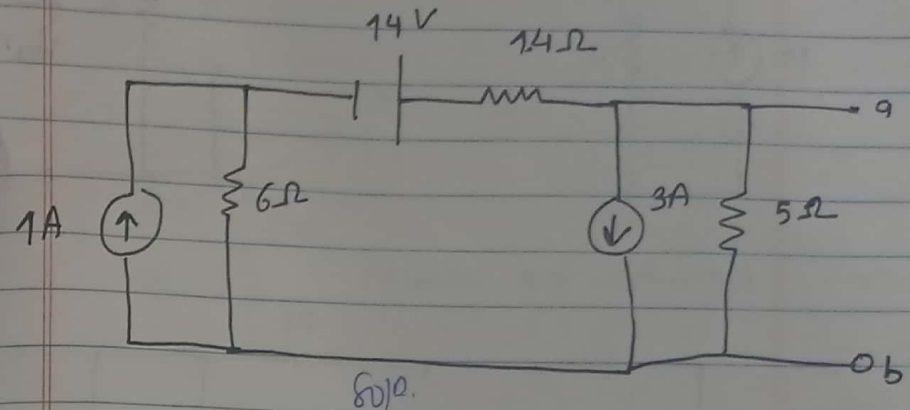
<Num.No.56> Find the Thevenin's and Norton's equivalent circuit terminals a-b.




Step 1/2:

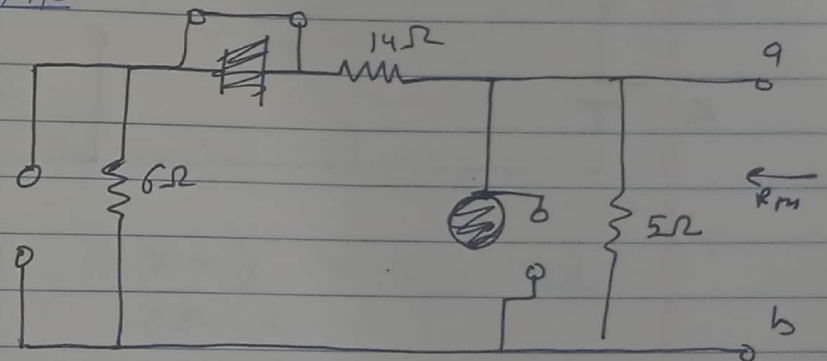


$$R_{TH} = (6 + 14) \parallel 5$$

$$= \frac{20 \times 5}{25} = 4\Omega$$

Considering 1 A current,

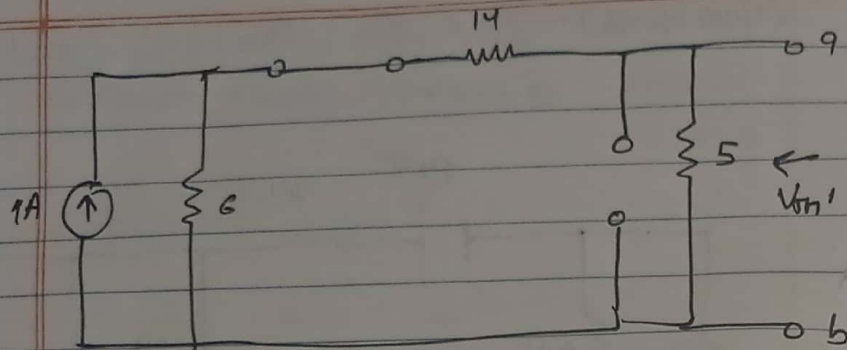


Redrawing the circuit,

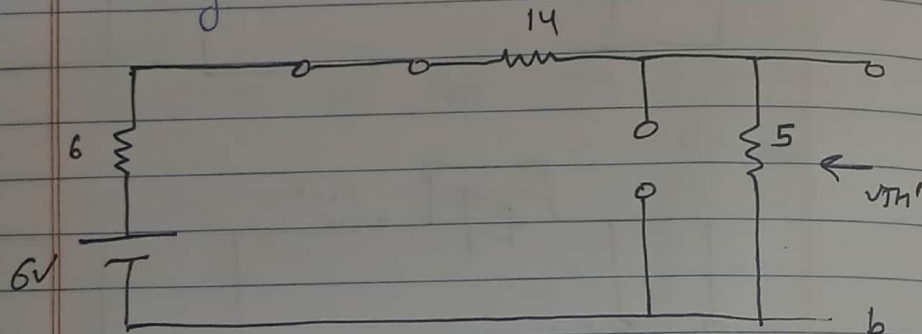


$$V_{5\Omega} = V_{TH}' = \frac{6 \times 5}{25} = 1.2V$$

Considering $3A$ current source,

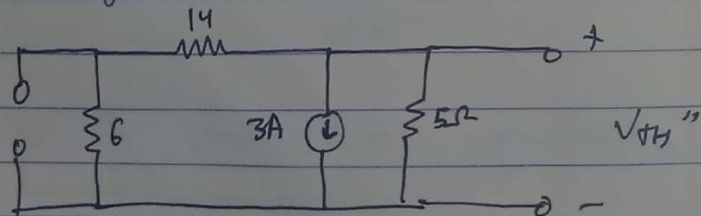

$$V_{5\Omega} = V_{TH}'' = \frac{20}{25} \times (3 \times 5) = -12V$$

Considering $14V$ voltage source.

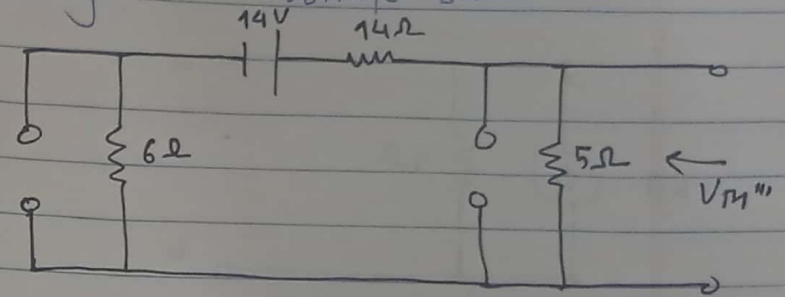


$$V_{5\Omega} = \frac{5 \times 14}{25} = 2.8V = V_{TH}'''$$

So,

$$V_{TH} = 1.2 - 12 + 2.8 = -8V$$

The equivalent Thevenin's circuit is,

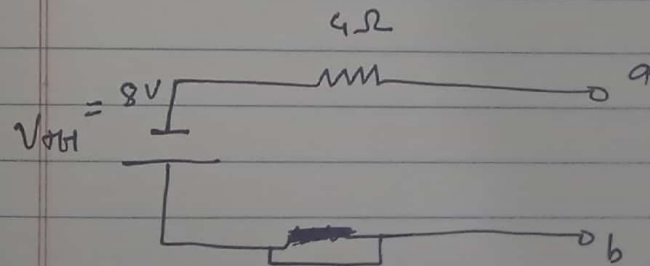

The equivalent Norton's circuit is,

$$I_N = \frac{8V}{4} = 2A.$$

$$R_N = R_{TH} = 4\Omega$$

