

Now,

$$I_{R3} = I_1 = 0.985 \text{ mA} \quad (\uparrow)$$


$$I_{R1} = I_1 - I_2 = 0.980 + 0.520 = 1.5 \text{ mA} \quad (\downarrow)$$

$$I_{R4} = I_2 = -0.520 \text{ mA} \quad (\rightarrow)$$

$$I_{R5} = I_2 - I_3 = -0.520 + 0.753 = 0.233 \quad (\downarrow)$$

$$I_{R2} = I_3 = 0.753 \text{ mA} \quad (\downarrow)$$

<Num. No. 38>: Find the branch current

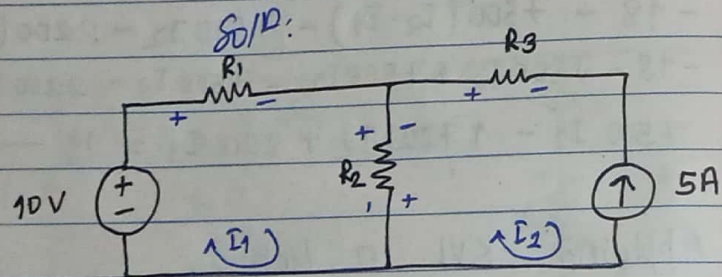

Given

$$R_1 = 4 \Omega$$

$$R_2 = 6 \Omega$$

$$R_3 = 3 \Omega$$

Here,

$$I_2 = -5 \text{ A} \quad (\because \text{presence of current source})$$

$$\therefore I_{R3} = -5 \text{ A} \quad (\rightarrow)$$

For loop 1,

$$+10 - I_1 R_1 - (I_1 - I_2) R_2 = 0$$

$$\text{or, } +10 - 4I_1 - 6(I_1 - I_2) = 0$$

$$\text{or, } 10 - 4I_1 - 6I_1 + 6I_2 = 0$$

$$\text{or, } -10I_1 + 6I_2 = -10$$


$$\text{or, } -10I_1 = 20$$

$$\therefore I_1 = -2 \text{ A}$$

$$\therefore I_{R1} = I_1 = -2 \text{ A} \quad (\rightarrow)$$

$$\begin{aligned} \therefore I_{R2} &= I_1 - I_2 \\ &= -2 + 5 = 3 \text{ A} \quad (\downarrow) \end{aligned}$$

<Num. No. 39>: Find the branch current.

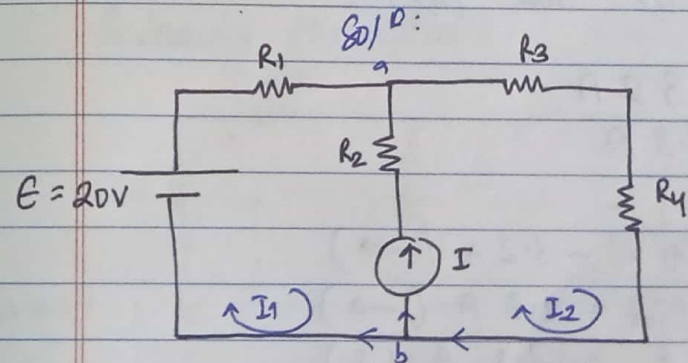

Given,

$$R_1 = 6 \Omega$$

$$R_2 = 2 \Omega$$

$$R_3 = 10 \Omega$$

$$R_4 = 4 \Omega$$


$$I = 6 \text{ A}$$

At node b, applying KCL,

$$I + I_1 = I_2$$

$$\text{or, } 6 = -I_1 + I_2 \quad \text{--- (i)}$$

Redrawing the circuit,

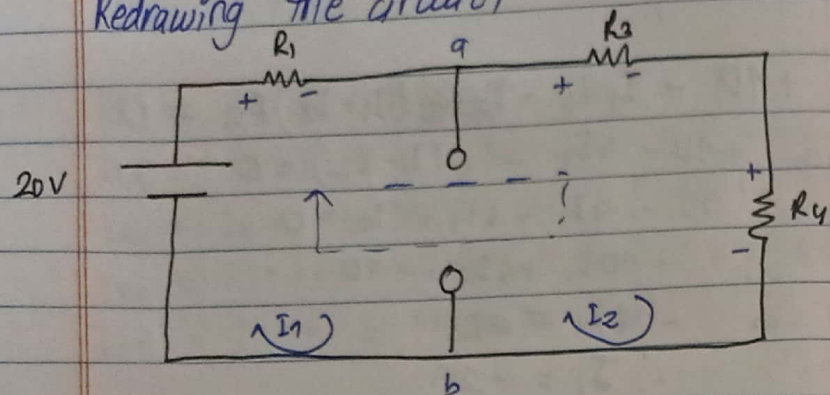

Applying KVL,

$$+20 - I_1 R_1 - I_2 R_3 - I_2 R_4 = 0$$

$$\text{or } 20 - 6I_1 - 10I_2 - 4I_2 = 0$$

$$\text{or } -6I_1 - 14I_2 = -20$$

$$\text{or } 6I_1 + 14I_2 = 20 \quad \text{--- (ii)}$$

Solving (i) and (ii),

$$I_1 = -3.2 \text{ A}$$

$$I_2 = 2.8 \text{ A}$$

$$I_{R1} = I_1 = -3.2 \text{ A} (\rightarrow)$$


$$I_{R3} = I_2 = 2.8 \text{ A} (\rightarrow)$$

$$I_{R4} = I_2 = 2.8 \text{ A} (\downarrow)$$

\*): This question, the battery is charging.

(Num. No. 40): Determine the current of network.

Soln.

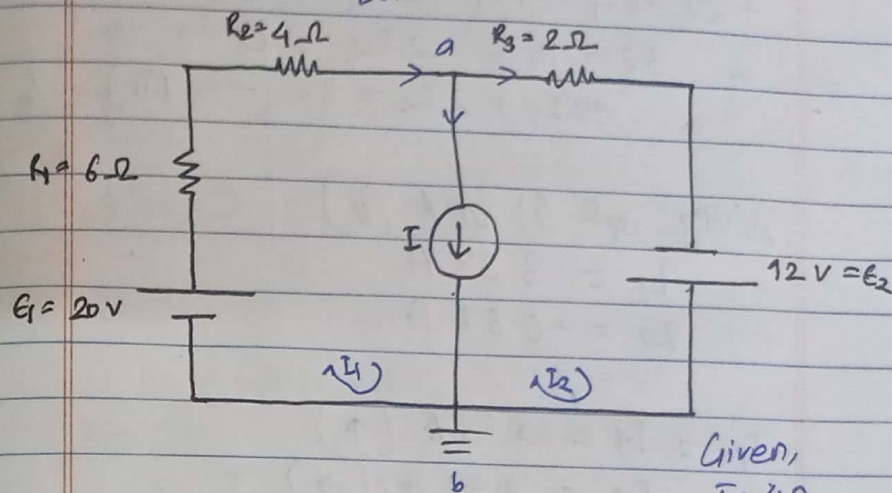


Given,  
 $I = 4 \text{ A}$ .

At node a,

$$I_2 + I = I_1$$

$$\text{or, } 4 = I_1 - I_2 \quad \text{--- (i)}$$

Redrawing the circuit,

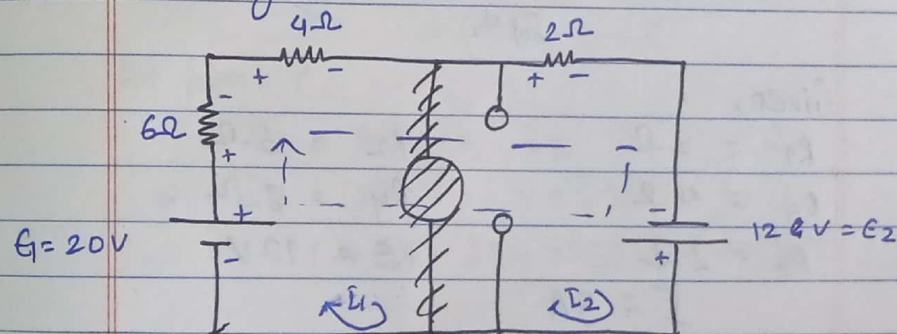



Applying KVL,

$$+20 - 6I_1 - 4I_1 - 2I_2 + 12 = 0$$

$$\text{or } 32 - 10I_1 - 2I_2 = 0$$

$$\text{or } 10I_1 + 2I_2 = 32 \quad \text{--- (ii)}$$

Solving eq<sup>n</sup> (i) and (ii)

$$I_1 = 3.33 \text{ A}$$

$$I_2 = -0.67 \text{ A}$$

$$I_{R1} = I_1 = 3.33 \text{ A } (\uparrow)$$

$$I_{R2} = I_1 = 3.33 \text{ A } (\rightarrow)$$

$$I_{R3} = I_2 = -0.67 \text{ A } (\rightarrow)$$

<Num. No. 41>: Find the  $I_1$  to  $I_4$  using

Mesh analysis.

Sol<sup>n</sup>:

Given,

$$R_1 = 2 \Omega$$

$$R_2 = 6 \Omega$$


$$R_3 = 4 \Omega$$

$$R_4 = 8 \Omega$$

$$R_5 = 2 \Omega$$

$$E = 10 \text{ V}$$

$$I = 5 \text{ A}$$

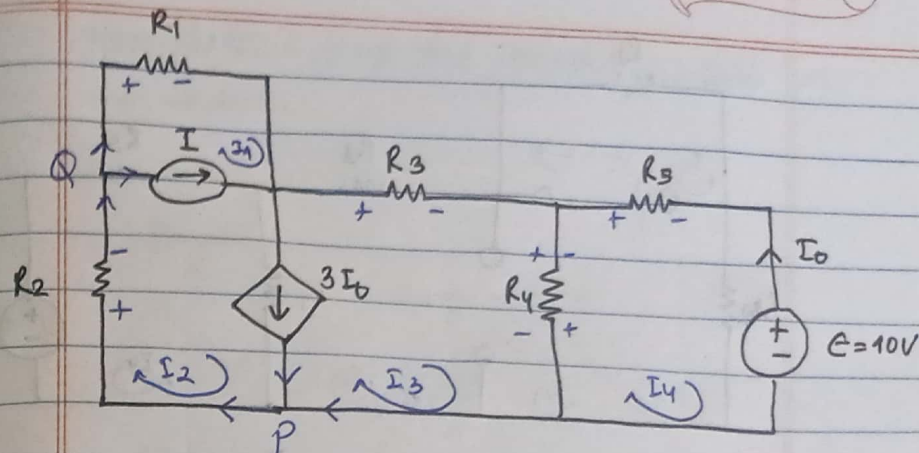

Here, for loop 4,

$$I_0 = -I_4$$

So,

$$3I_0 = -3I_4$$

At point Q,  $I_1 + I = I_2$

$$\text{or, } I = I_2 - I_1$$

$$\text{or } -I_1 + I_2 = 5 \quad \text{--- (i)}$$

$$\text{or } I_2 = 5 + I_1 \quad \text{--- (a)}$$


At point P,

$$I_3 + 3I_0 = I_2$$

$$\text{or, } I_3 - 3I_4 = 5 + I_1$$

$$\text{or } -I_1 + I_3 - 3I_4 = 5 \quad \text{--- (b)}$$

Redrawing the circuit, we get.

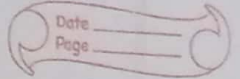

Applying KVL,  
 ~~$2I$~~  for loop 1.

For loop  $\uparrow$ ,

$$-I_1 R_1 - I_2 R_2 - I_3 R_3 - (I_3 - I_4) R_4 = 0$$

$$\alpha_1 \quad -2I_1 - 6I_2 - 4I_3 - 8I_4 + 8I_5 = 0$$

$$-2I_1 - 6I_2 - 12I_3 + 8I_4 = 0 \quad \text{--- (c)}$$

for loop 2,

$$-10 - (I_4 - I_3)R_4 - I_4 R_5 = 0$$

$$-10 - (I_4 - I_3) 8 - 2I_4 = 0$$

$$\text{or, } 8I_3 - 10I_4 = 10 \quad \text{--- (d)}$$

solving, we get.

$$I_1 = -7.5 \text{ A}$$


$$I_3 = 3.93 \text{ A}$$

$$I_2 = -2.5 \text{ A}$$

$$I_4 = 2.148 \text{ A}$$


⟨Num. No 42⟩ Find the resistance  $R_{ab}$  on the circuit.

Soln:

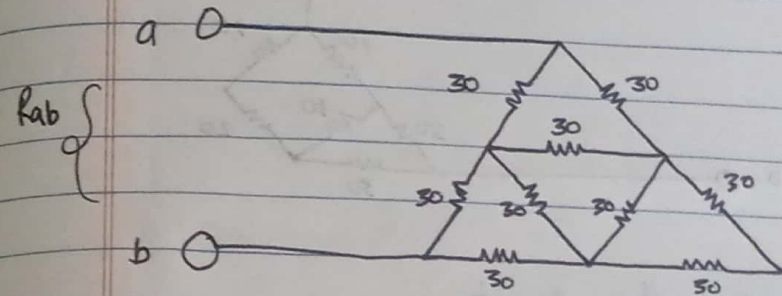


Now,

Redrawing the circuit.

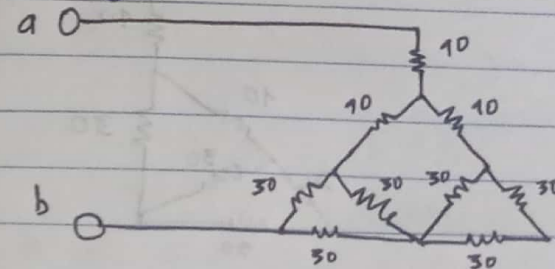


Redrawing the circuit,

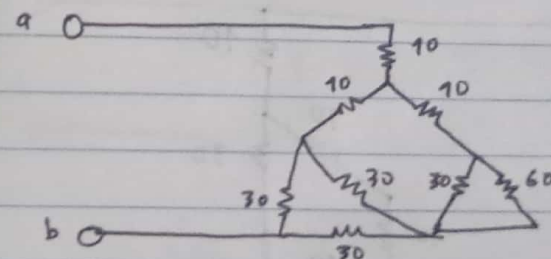





Redrawing the circuit,

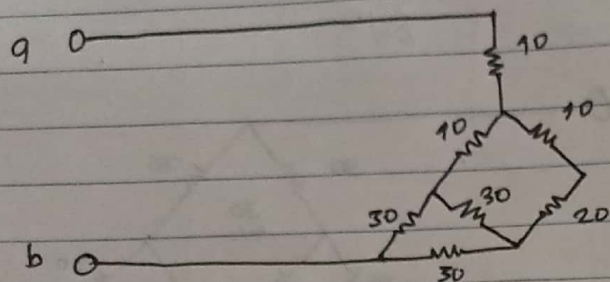


Redrawing the circuit,

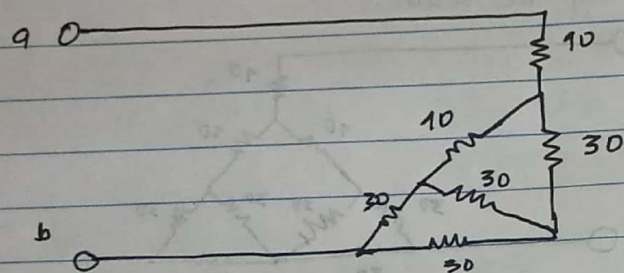


Redrawing the circuit,

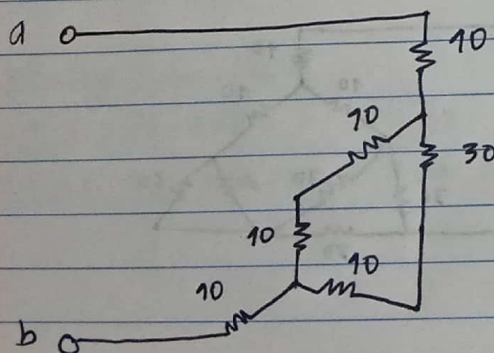


Redrawing the circuit,

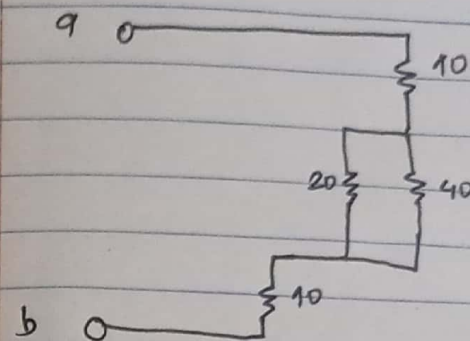

Redrawing the circuit,

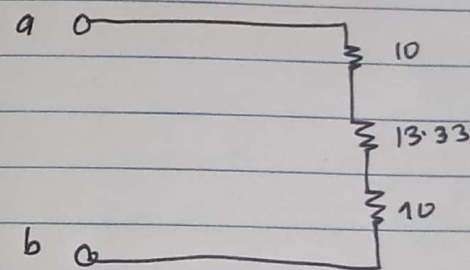

Redrawing the circuit,

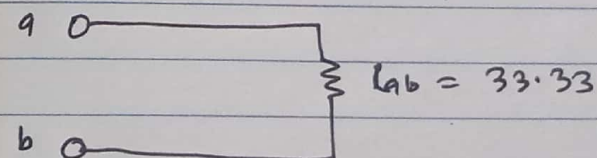

$$\therefore R_{ab} = 33.33 \, \Omega$$