

At node 3,

$$\frac{V_3 - V_2}{2} + \frac{V_3}{2} + \frac{V_3 - 20}{4} = 0$$

$$\text{or, } \frac{V_3 - V_2}{2} + \frac{V_3}{2} + \frac{V_3}{4} - \frac{20}{4} = 0$$

$$\text{or, } -\frac{V_2}{2} + \frac{5V_3}{4} = 5 \quad \text{--- (iii)}$$

$$\text{or, } -2V_2 + 5V_3 = 20 \quad \text{--- (iii')}$$

Solving (i), (ii), (iii), we get.


$$V_1 = -6.41 \text{ V}$$

$$V_2 = -2.825 \text{ V}$$

$$V_3 = 2.87 \text{ V}$$

~~Num. No. 48/49/50~~ ~~1st numerical solved~~
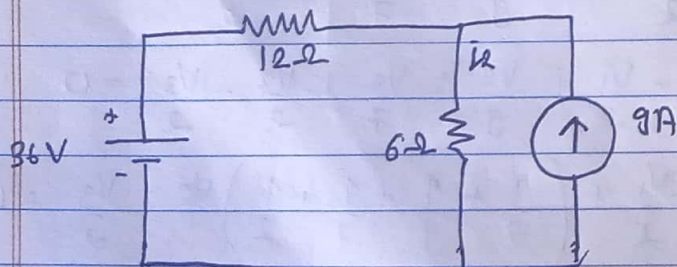
<Num. No. 48>: Find the current I_2 using superposition theorem.




Step 1: Consider the source voltage $E = 36 \text{ V}$ and replace current source with open circuit.

Now,

$$I_2' = \frac{E}{R_1 + R_2}$$

$$= \frac{36}{18}$$

$$\therefore I_2' = 2 \text{ A (↓)}$$

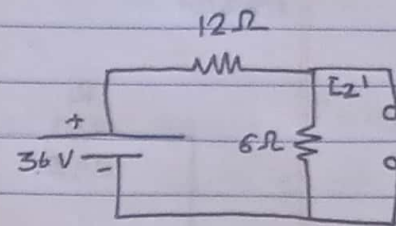


Step 2: Consider the current source $I = 9 \text{ A}$, replacing voltage source with short circuit.

Here,

$$R_{eq} = 12 \parallel 6$$
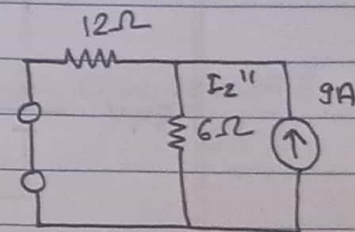
$$= \frac{12 \times 6}{12 + 6} = 4 \Omega$$



$$\therefore I_2'' = 9 \times \frac{4}{12} = 3 \text{ A (↓)}$$


Now,

$$I_2 = I_2' + I_2''$$


$$= 2 + 3 = 5 \text{ A}$$

Num. No. 49: Using superposition theorem, determine the current through 12Ω resistor.

Soln:

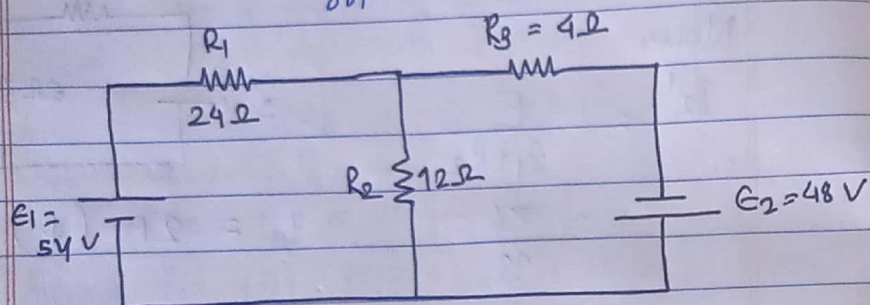

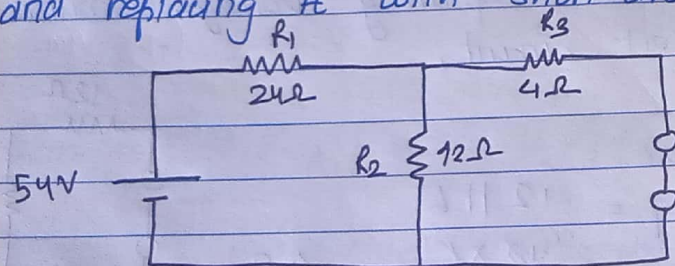Step 1: Consider the voltage source $E = 54V$ and replacing ~~it~~ ^{another} with short circuit,



Here,

$$R_{eq} = 24 + (12 \parallel 4) = 24 + \frac{12 \times 4}{16} = 27\Omega$$


Then,

$$I = \frac{E_1}{R_{eq}} = \frac{54}{27} = 2A$$

Now

$$\therefore I_{12\Omega}' = \frac{I \times R_3}{R_2 + R_3} = \frac{2 \times 4}{16} = 0.5 \text{ (}\downarrow\text{)}$$

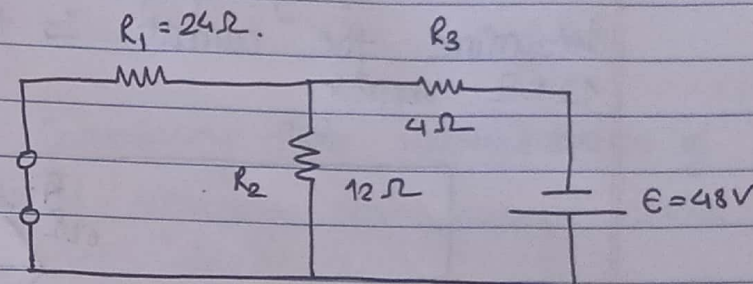Step 2: Consider the voltage source $E = 48V$ and replacing ~~with~~ another with short circuit,



Here,

$$R_{eq} = 4 + (12 \parallel 24) = 4 + \frac{12 \times 24}{36} = 12\Omega$$

$$\therefore R_{eq} = 12\Omega$$

$$I = \frac{V}{R_{eq}} = \frac{48}{12} = 4A$$

Now,

$$I_{12\Omega}'' = \frac{I \times R_1}{R_2 + R_1} = \frac{4 \times 24}{36} = 2.67A \text{ (}\uparrow\text{)}$$

Then,


$$I_{12} = I_{12}'' - I_{12}'$$

$$= 2.67 - 0.5$$


$$\therefore I_{12} = 2.17 \text{ (A)} \quad (\uparrow)$$

<Num.No-50>:- Using superposition theorem, determine the current I_2 through $12 \text{ k}\Omega$ resistor.

Soln.

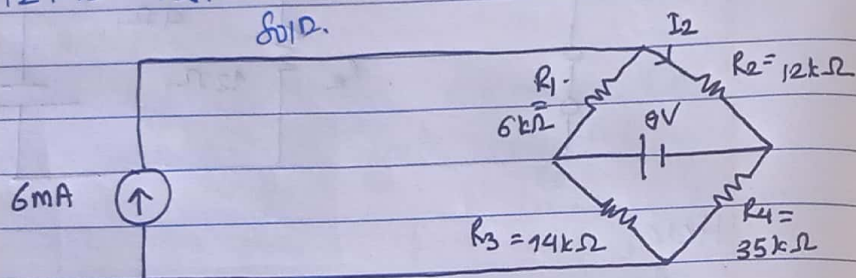

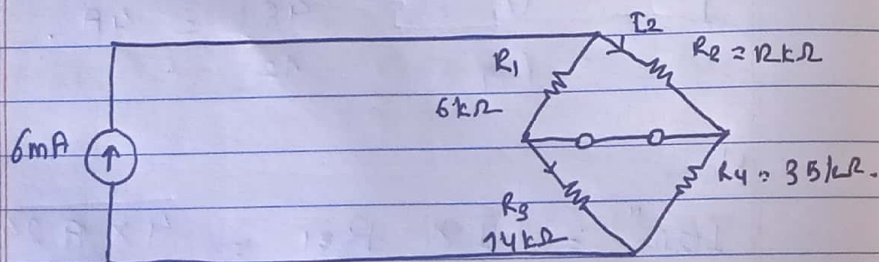Step 1: Replacing the 9 V voltage source by a short circuit considering 6 mA current source.




Using current divider rule,

$$I_{2}' = \frac{I \times R_1}{R_1 + R_2}$$

$$= \frac{6 \text{ mA} \times 12}{12 + 6} = \frac{2 \times 6}{18}$$

$$\therefore I_{2}' = 2 \text{ mA} \quad (\downarrow)$$

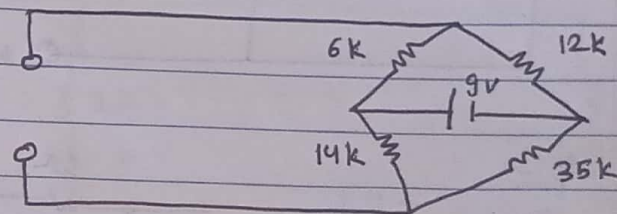Step 2: Considering the voltage source of 9 V and replacing the current source with open circuit.



Here,

$$R_{eq} = (6 + 12) \parallel (14 + 35)$$


$$= \frac{18 \times 49}{18 + 49} = 13.16 \text{ k}\Omega$$

$$\text{Now, } I_2'' = \frac{V}{R_{eq}} = \frac{9}{13.16} = 0.5 \text{ mA} \quad (\downarrow)$$


$$\text{Then, } I_2 = I_2' + I_2'' = 2 + 0.5 = 2.5 \text{ mA}$$

<Num.No.51>: Find the Thevenin's equivalent circuit for the network in figure marked by a and b point.

Solⁿ:

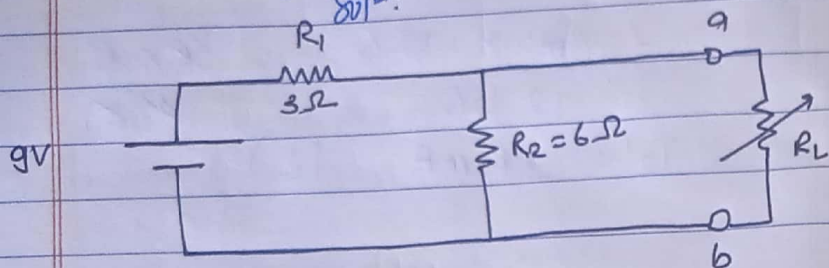

Step 1/2:

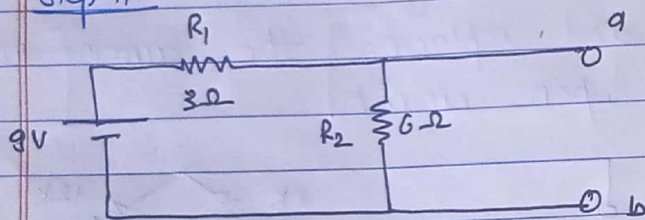


Step 3:

$$R_{TH} = 3 \parallel 6$$

$$= \frac{3 \times 6}{3 + 6}$$


$$= 2 \Omega$$

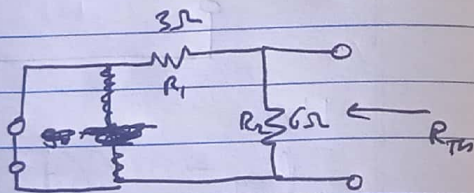

Step 4:


$$V_{TH} = V_{ab} = \frac{9 \times 6}{6 + 3} = 6 \text{ V}$$

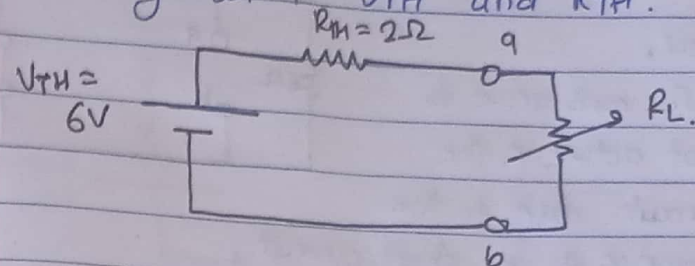Step: 5 The Thevenin equivalent circuit redrawing with V_{TH} and R_{TH} .




<Num.No.52>: Find the Thevenin's equivalent circuit for the network between point a & b.

Solⁿ:

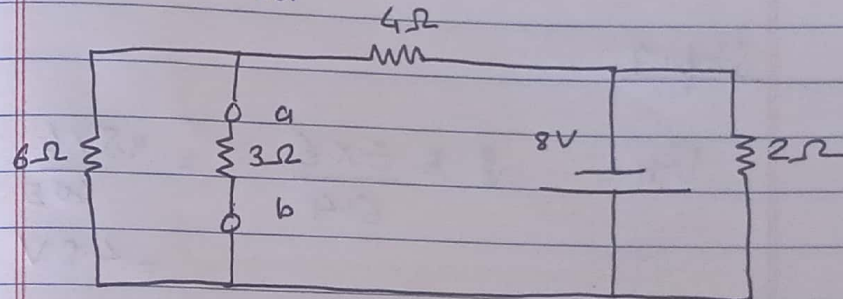


Step 1/2:

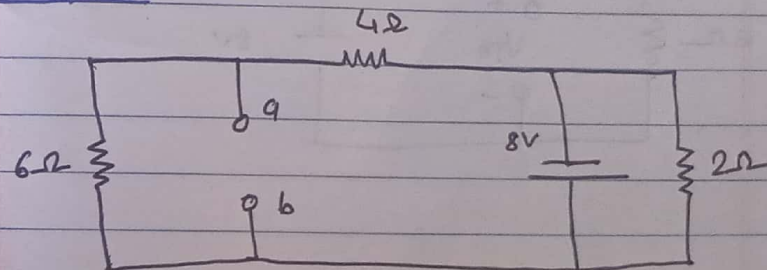

Step: 3:

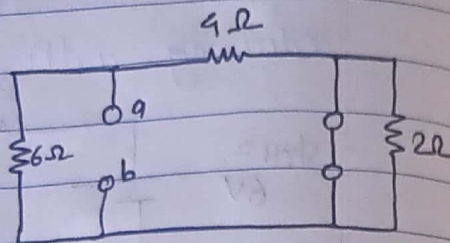
Here,
 2Ω resistance is
 not active in the
 circuit due to the
 presence of a short circuit,



$$R_{TH} = \frac{6 \parallel 4}{10} = \frac{6 \times 4}{10} = 2.4 \Omega$$

Step: 4
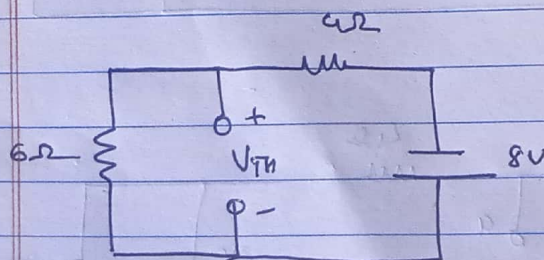
$$V_{TH} = \frac{E \times 6}{6+4} = \frac{48 \times 6}{10} = 4.8 V$$



Using

Step: 5: V_{TH} and R_{TH} , drawing the
 equivalent Thevenin's circuit,

