

PHYSICS PRACTICAL SHEETS

Date 29 August 2023

KV CAMPUS

Class CE

Roll No. 25

Shift Day

Experiment No. 7

Group T

Sub. PHY102

Set

Object of the Experiment (Block Letter)

STUDY OF PHENOMENON OF RESONANCE IN PARALLEL LCR CIRCUIT

Apparatus Required:

- i) Frequency generator
- ii) Inductor and resistor
- iii) Capacitor box
- iv) Multimeter
- v) AC supply.

Theory

The impedance Z for parallel LCR circuit is

$$Z = \frac{R + i\omega [L(1 - \omega^2 LC) - CR^2]}{[(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2]}$$

where, $Z = |Z|e^{i\theta}$ is complex quantity.

$|Z|$ = impedance of circuit θ = phase difference betⁿ voltage & I

It can be shown that,

$$\tan \theta = \omega [L(1 - \omega^2 LC) - CR^2] / R$$

The impedance as well as the phase difference betⁿ source voltage and current depends on frequency. At resonant frequency,

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}, \text{ the impedance becomes maximum resulting minimum current in circuit.}$$

When R is small then, $1/LC \gg R^2/L^2$ and Hence,

$$f_0 = \sqrt{\frac{1}{LC}} \times \frac{1}{2\pi}$$

Let us consider a slightly modified // circuit with high resistance R_s ($R_s \gg Z$) connected to the source in series. Keeping the source voltage constant (V_{rms}), the impedance Z of the // circuit changes resulting the change in current in the circuit. Since $R_s \gg Z$, the change in current due to change in impedance is negligibly small. It turns out that with change in frequency, the I_{rms} in the circuit remains almost constant but the voltage across the LC parallel changes.

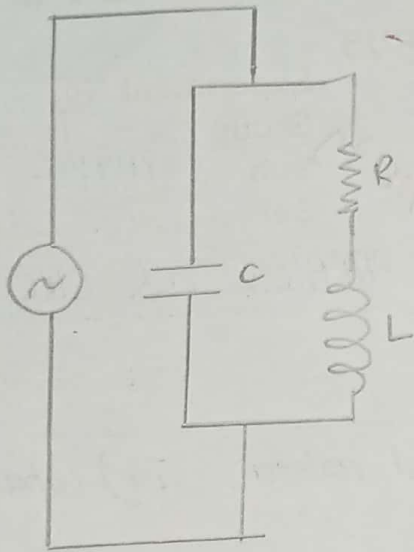


Fig. Diagram of || LCR with AC source.

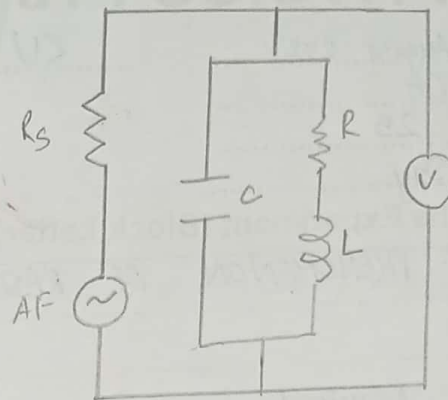


Fig. Diagram || LC circuit with AC source with high resistance in series.

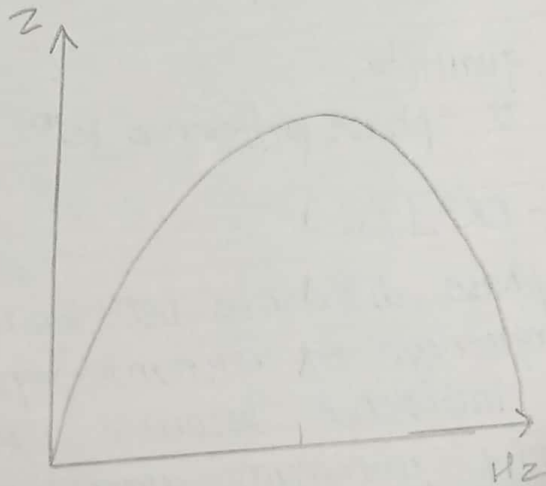


Fig. Z vs Hz graph

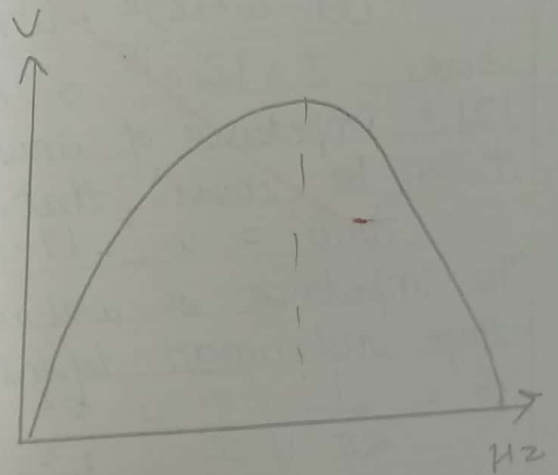


Fig. Z vs Hz graph

Observations:

No of obs	$C_1 = 0.1 \mu F$		$C_2 = 0.22 \mu F$		$C_3 = 0.33 \mu F$	
	f (Hz)	V (voltage)	f (Hz)	V (voltage)	f (Hz)	V (Voltage)
1	0	0	0	0	0	0
2	1000	0.9	1000	1	1000	1.1
3	2000	1.8	2000	2.2	2000	2.5
4	3000	2.5	3000	3.05	3000	2.7
5	4000	3.1	4000	3.1	3200	2.6
6	5000	3.6	4400	2.9	3600	2.35
7	6000	3.65	4800	2.55	4000	2.05
8	6600	3.7	5000	2.4	5000	1.35
9	7000	3.6	6000	1.75	6000	1.35 0.85
10	7200	3.4	7000	1.2	7000	0.85
11	8000	3.1	8000	0.8	8000	0.55 0.33
12	9000	2.4	9000	0.6	9000	0.32
13	10000	1.9	10000	0.4	10000	0.1
14	11000	1.4	11000	0.3	11000	0.1
15	12000	1.1	12000	0.2	12000	0
16	13000	0.8	13000	0.1		
17	14000	0.6	14000	0.1		
18						

x) Calculation of induction:

No of obs	Capacitance (μF)	Resonant frequency (Hz)	Inductance (mH)
1	0.1	6600	5.81 10.3
2	0.22	4000	3000 7.19
3	0.33	3000	8.52

\therefore Mean inductance (H) = 7.17 mH

x) Result:


The value of the given inductor is 7.17 mH

(x) Precautions:

- i) Circuit connection must be well checked before joining the AC supply.
- ii) The connecting wires should be checked using multimeters.


$f_{0.1} = 0.1 \text{ MHz}$

Amplitude
 $10 \text{ cm/div} = 100 \text{ mV}$
 $1 \text{ cm/div} = 10 \text{ mV}$

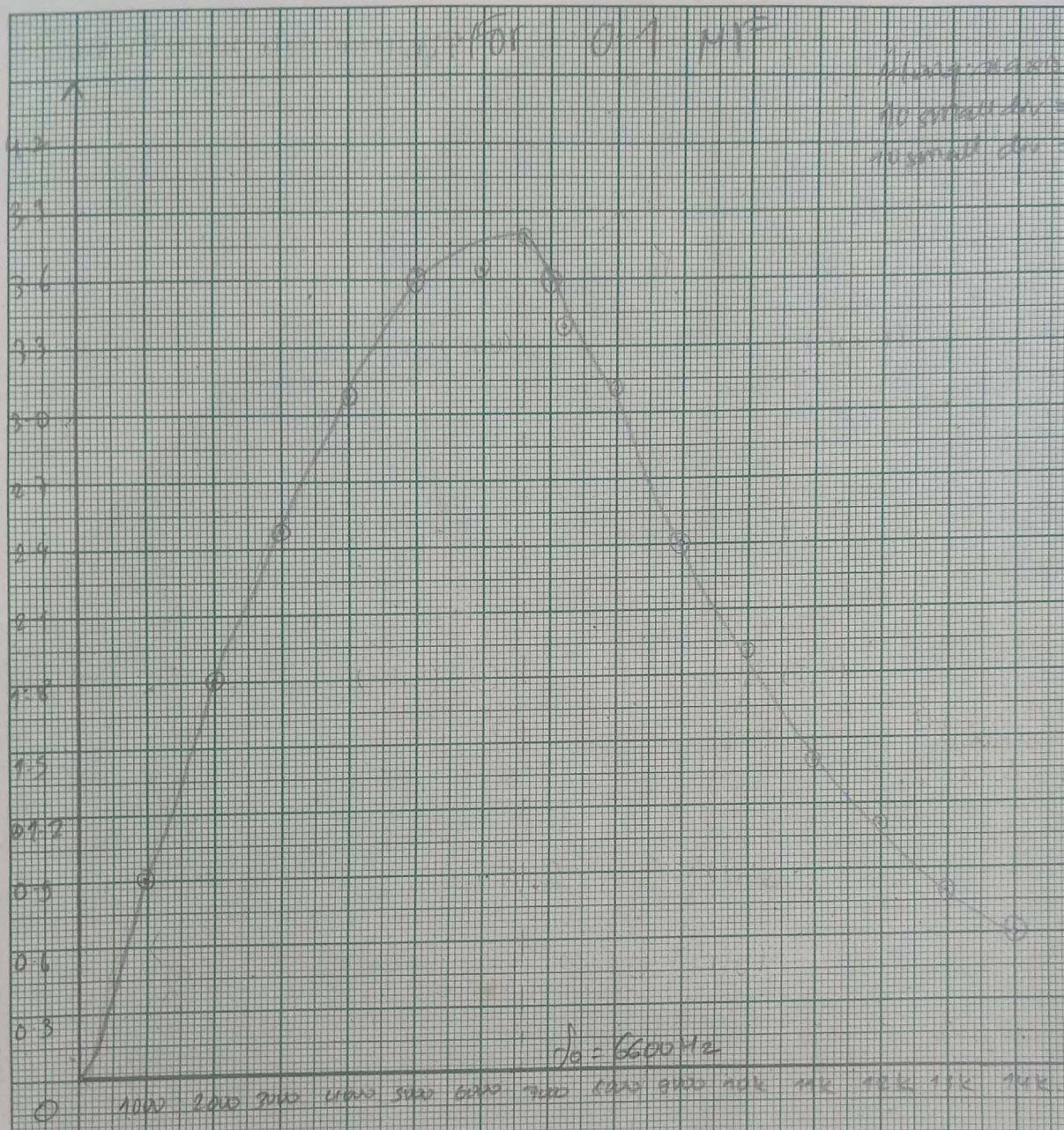

for 0.22 MF

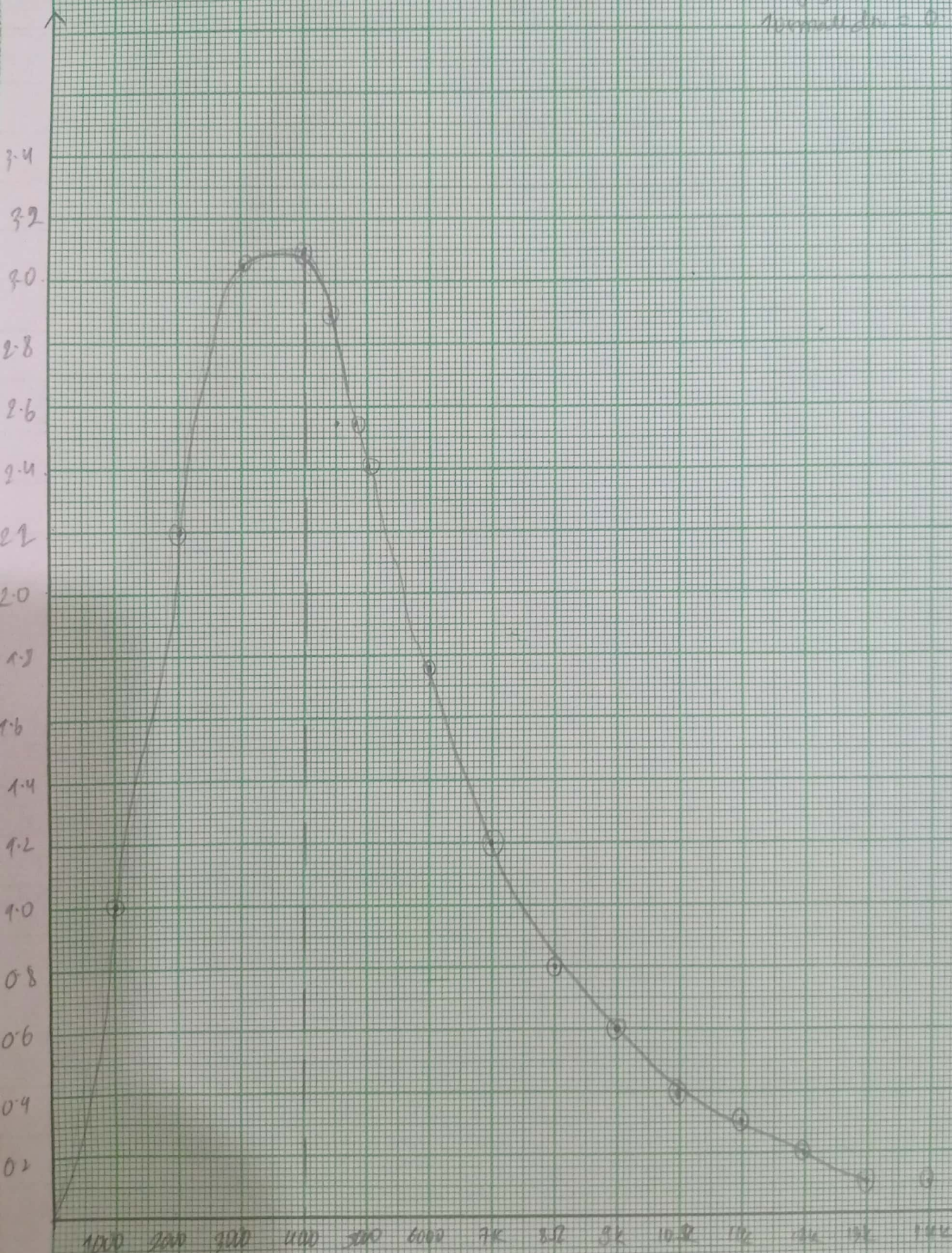Along x-axis
10 small div = 1000 Hz
Along y-axis
10 small div = 0.2 V



$f_0 = 4000$

for $0.33 \mu F$

Along x-axis
10 small div = 1000 Hz
Along y-axis
10 small div = 0.2 V

