

<Num-No-6>: Determine the current through a $5\text{ k}\Omega$ resistor when the power dissipated is 20 mW .

Solⁿ:

Given,

$$\text{Resistance (R)} = 5\text{ k}\Omega \\ = 5000\ \Omega$$

$$\text{Power (P)} = 20\text{ mW} \\ = 200 \times 10^{-3}\text{ W}$$

Current (I) = ?


We know,

$$P = I^2 R$$


$$\text{or, } \sqrt{\frac{P}{R}} = I \quad \text{or, } I = \sqrt{\frac{200 \times 10^{-3}}{5000}}$$

$$= 2 \times 10^{-3}\text{ A}$$

$$\therefore I = 2\text{ mA}$$

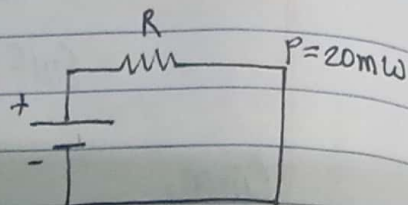
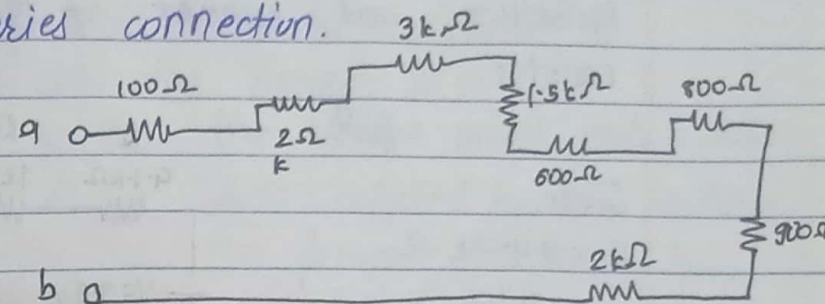
<Num-No-7>: Determine the total resistance of series connection.




Solⁿ:

In the diagram, we need to imaginary voltage source.

Since the same current flows through the circuit, the equivalent resistance is the sum of the resistance of all resistors.

Now,
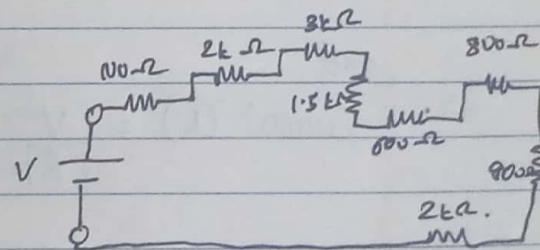
$$R_T = R_1 + R_2 + R_3 \\ + R_4 + R_5 + R_6 + \\ R_7 + R_8$$



$$= 100\ \Omega + 2000\ \Omega + 3000\ \Omega + 1500\ \Omega + 600\ \Omega + 800\ \Omega + 900\ \Omega \\ + 2000\ \Omega$$

$$= 10,900\ \Omega = 10.9\text{ k}\Omega$$

(Num-No-8): Determine the total resistance and current of the series resistor.

Solⁿ:

Given,

$$R_1 = 4.7 \text{ k}\Omega = 4700 \Omega$$

$$R_2 = 1 \text{ k}\Omega = 1000 \Omega$$

$$R_3 = 2.2 \text{ k}\Omega = 2200 \Omega$$

$$R_4 = 1 \text{ k}\Omega = 1000 \Omega$$

$$R_5 = 1 \text{ k}\Omega = 1000 \Omega$$


Now,

$$\begin{aligned} \text{Total resistance } (R_T) &= R_1 + R_2 + R_3 + R_4 + R_5 \\ &= 9.9 \text{ k}\Omega = 9900 \Omega \end{aligned}$$

and

$$\text{Current } (I) = \frac{V}{R_T} = \frac{9.9}{9900} = 10^{-3} \text{ A}$$


$$\therefore I = 1 \text{ mA}$$

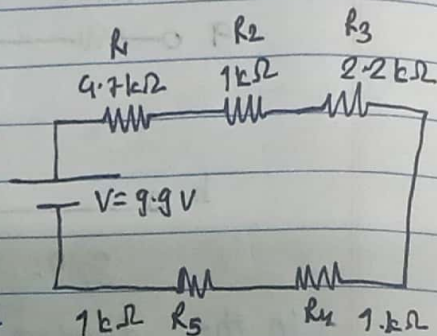

(Num-No-9): For the series circuit,

- i) Determine the total resistance R_T
- ii) Calculate the current I_s
- iii) Determine the voltage across each resistor.
- iv) Find the power supplied by the battery.
- v) Determine the power dissipated by each resistor.

Solⁿ:

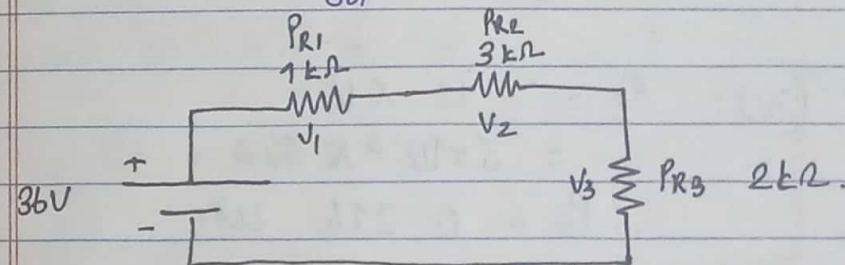

Solⁿ:

Given,

$$\text{voltage } (V) = 36 \text{ V}$$

$$\text{resistance } (R_1) = 1 \text{ k}\Omega$$

$$\text{resistance } (R_2) = 3 \text{ k}\Omega$$

$$\text{resistance } (R_3) = 2 \text{ k}\Omega$$

Now,

$$\text{i) Total resistance } (R_T) = R_1 + R_2 + R_3 = 6 \text{ k}\Omega = 6000 \Omega$$

$$\text{ii) } V = I_s \times R_T$$

$$\text{on } I_s = \frac{36}{6000} = 6 \text{ mA} = 6 \times 10^{-3} \text{ A}$$

(iii): $V_1 = I_s \times R_1$
 $= 6 \times 10^{-3} \times 1000 = 6 \text{ V}$

$V_2 = \cancel{6 \times 10^{-3}} I_s \times R_2$
 $= 6 \times 10^{-3} \times 3000 = 18 \text{ V}$

$V_3 = I_s \times R_3$
 $= 6 \times 10^{-3} \times 2000 = 12 \text{ V}$

(iv): $P_E = I_s \times V$
 $= 6 \times 10^{-3} \times 36$
 $\therefore P_E = 0.216 \text{ W}$

(v): $P_{R1} = V_1^2 / R_1$
 $= (6)^2 / 1000 = 0.036 \text{ W}$

$P_{R2} = V_2^2 / R_2$
 $= (18)^2 / 3000 = 0.108 \text{ W}$

$P_{R3} = V_3^2 / R_3$
 $= (12)^2 / 2000 = 0.072 \text{ W}$

< Num. No. 107: Determine the total voltage and polarity.

Soln:


We know

$\sum \uparrow V = 0$

or, $V_3 - V_2 + V_1 = 0$

or, $V_3 - V_2 + V_1 - V_T = 0$

$V_T = 4 \text{ V}$

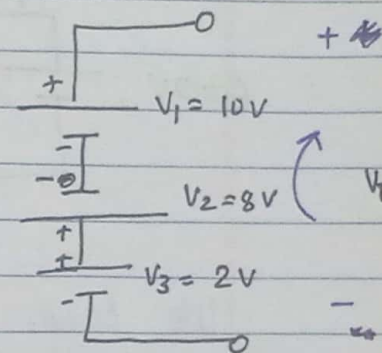


$\sum \uparrow V = 0$

or, $-V_4 + V_3 - V_2 + V_1 + V_T = 0$


or, $-10 + 8 - 6 + 5 + V_T = 0$

$\therefore V_T = 3 \text{ V}$

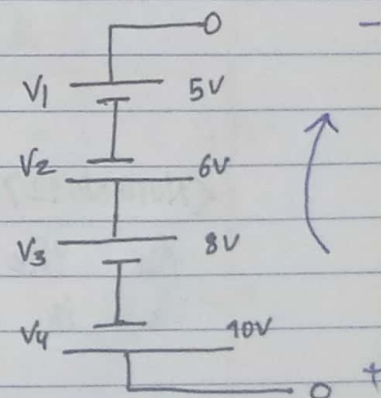

< Marked in blue is our supposition >
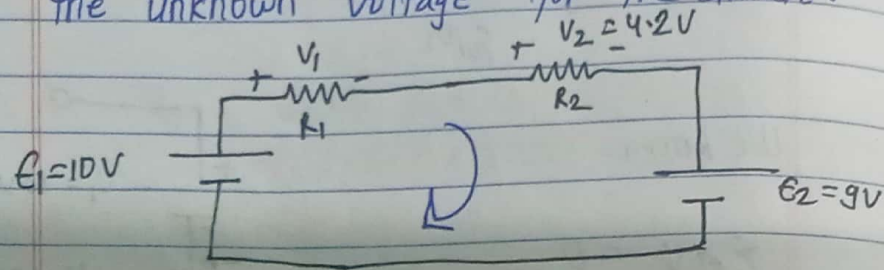
<Num. No-11>: Use KVL to determine the unknown voltage for the circuit.



Solⁿ:

We know, from KVL,

$$\sum V = 0$$


$$\text{or, } +10 - V_1 - V_2 - 9 = 0$$

$$\text{or, } 10 - 4.2 - 9 = 0$$

$$\therefore V = -3.2V$$

<Num No12>: Determine the voltage V_x for the circuit. Note polarity of V_x is not provided.

Solⁿ:

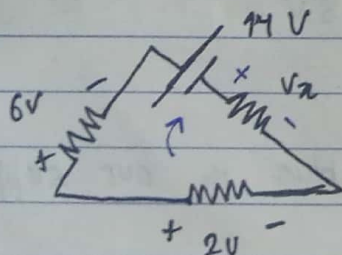

Using KVL,
we know,


$$\sum V = 0$$

$$\text{or, } -6 - 14 - V_x + 2 = 0$$

$$\therefore V_x = -18V$$

<Num. No-13>: Determine the unknown voltage for the circuit in figure.

Solⁿ:

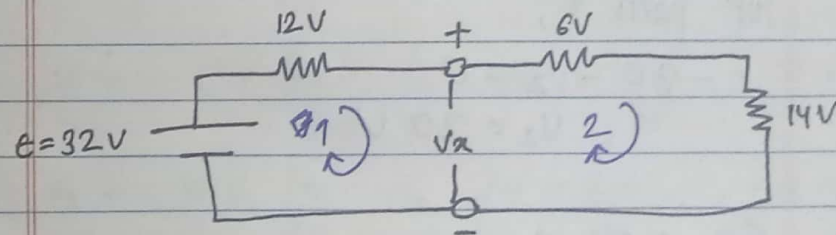

By path 1,

$$+32 - 12 - V_x = 0$$

$$\therefore V_x = 20V$$


By path 2,

$$-6 - 14 + V_x = 0$$

$$\therefore V_x = 20V$$

<Num No 14>: Determine V_1 and V_2 using KVL.

Sol D:

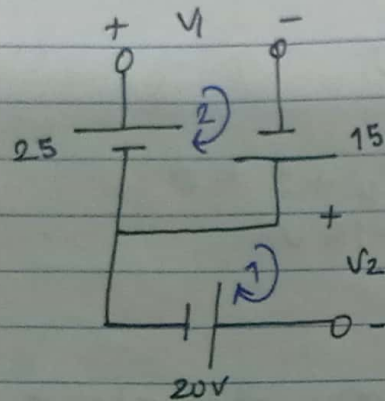

Using KVL,

For path 1,

$$-20 - V_2 = 0$$

$$\therefore V_2 = 20 \text{ V}$$

For path 2,

$$25 - V_1 + 15 = 0$$

$$\therefore V_1 = 40 \text{ V}$$

<Num No 15>: Find the voltage V_1 and V_2 by using voltage divider rule.


Sol D:

Given,

$$\text{total voltage } (V) = 64 \text{ V}$$

$$\text{resistance } (R_1) = 20 \Omega$$

$$(R_2) = 60 \Omega$$

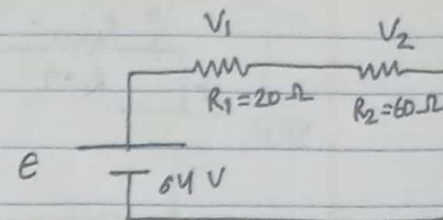

Let total resistance = R_T .

$$\therefore R_T = R_1 + R_2 = 80 \Omega$$


Using voltage divider rule,

$$V_1 = V \times \frac{R_1}{R_T} = 64 \times \frac{20}{80} = 16 \text{ V}$$

$$V_2 = V \times \frac{R_2}{R_T} = 64 \times \frac{60}{80} = 48 \text{ V}$$

<Num No 16>: Determine the current through the circuit and the voltage across the 7Ω resistor for the network.

Sol D:

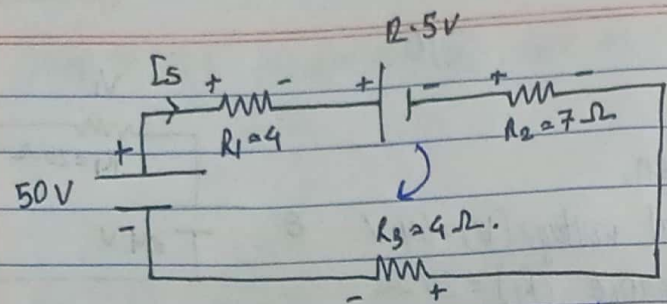

Let I_s be the current in the circuit.
Using KVL, we know,

$$\sum V = 0$$

$$\text{or, } +50 - V_1 - 12.5 - V_2 - V_3 = 0$$

$$\text{or, } 50 - 4 \times I_s - 12.5 - 7 \times I_s - 4 \times I_s = 0$$

$$\text{or, } 37.5 - 15 I_s = 0$$

$$\therefore I_s = 2.5 \text{ A}$$

Now

$$V_2 = I_s \times R_2$$

$$= 2.5 \times 7$$


$$\therefore V_2 = 17.5 \text{ V}$$

<Num No: 17>: For the network

a) find V_{ab}

b) find V_b

c) calculate V_c
8012:

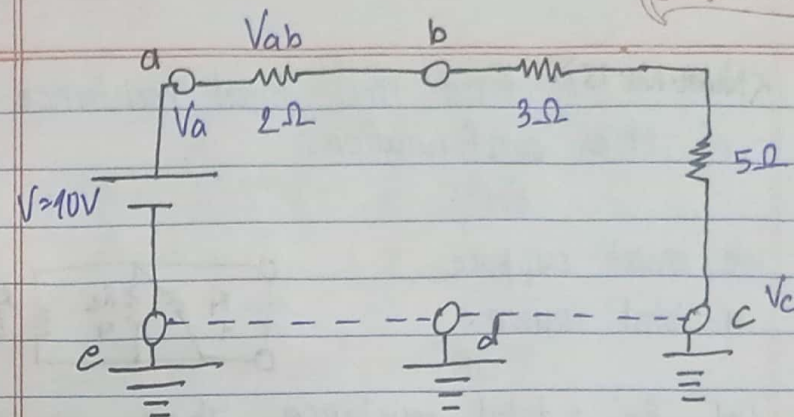

Since points c, d, e is on the ground, we can connect them.

$$\text{Total resistance } (R_T) = 3 + 2 + 5 = 10 \Omega$$

Using voltage single subscript and ~~multiple~~ double subscript rule.

$$(i): V_a = 10 \text{ V}$$

$$(ii): V_{ab} = R_1 \times \frac{V}{R_T} = 2 \times \frac{10}{10} = 2 \text{ V.}$$

801


$$V_{ab} = V_a - V_b$$

$$\text{or } 2 = 10 - V_b \quad \therefore V_b = 8 \text{ V}$$

$$(iii): V_c = 0 \quad (\because \text{grounded})$$

<Num. No. 18>: find the total resistance of the configuration.
solⁿ:

We must suppose a total source.

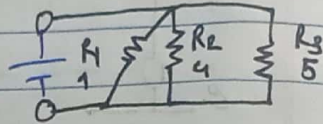

Let R_T = total resistance. Then,

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


$$\text{or } \frac{1}{R_T} = 1 + \frac{1}{4} + \frac{1}{5} = 1.45$$

$$\therefore R_T = 0.689 \Omega$$

<Num. No. 19>: For the parallel network

- find total resistance
- calculate the source current
- Determine the current through each resistor.

solⁿ:

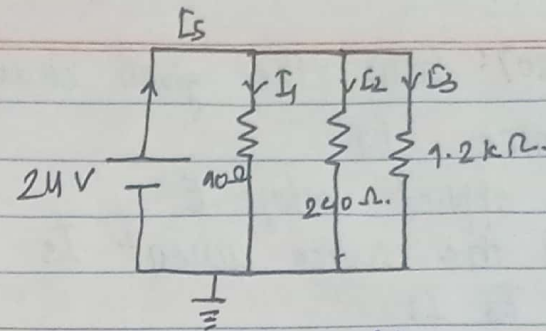

Let R_T = total resistance.

Then,

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\text{or } \frac{1}{R_T} = \frac{1}{10} + \frac{1}{240} + \frac{1}{1200} = 0.10$$

$$\text{i) } \therefore R_T = 9.48 \Omega$$

$$\text{ii) Thus, } \frac{V}{R_T} = I_s$$

$$I_s = \frac{24}{9.48} = 2.53 \text{ A}$$


$$\begin{aligned} \text{iii) } I_1 &= \frac{V}{R_1} = \frac{24}{10} = 2.4 \text{ A} & I_2 &= \frac{V}{R_2} = \frac{24}{240} = 0.1 \text{ A} & I_3 &= \frac{V}{R_3} = \frac{24}{1200} = 0.02 \text{ A} \end{aligned}$$

<Num.No.20>: From the given circuit.

- Determine R_3
- Find applied voltage E
- Find the source current I_s
- Find I_3 .

Soln:

Let R_T be the total resistance.

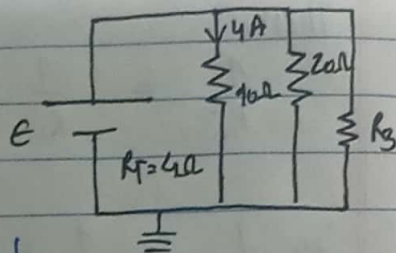

$$(i): \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\text{or } \frac{1}{R_3} = \frac{1}{4} - \frac{1}{10} - \frac{1}{20} \quad \therefore R_3 = 10 \Omega$$

$$(ii): \text{ We know } V_1 = I_1 \times R_1$$

$$\text{or } E = 4 \times 10 = 40 \text{ V}$$

$$(iii): I_2 = \frac{E}{R_2} = \frac{40}{20} = 2 \text{ A}$$

$$(iv): I_3 = I_s - I_1 - I_2 = 10 - 2 - 4$$

$$\therefore I_3 = 4 \text{ A}$$

$$(v): R_3 = \frac{E}{I_3} = \frac{40}{4} = 10 \Omega$$

<Num.No.21>: Determine the current I_3 and I_4 in figure using KCL.

Soln:


Using KCL,

$$I_1 + I_2 = I_3$$

$$\therefore I_3 = 5 \text{ A}$$

$$I_3 + I_5 = I_4$$

$$\therefore I_4 = 6 \text{ A}$$

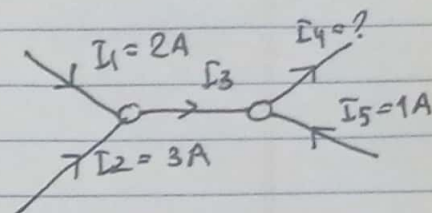


<Num.No.22>: Determine the ^{unknown} current.

Soln:

$$\text{We know}$$

$$I_A = I_1 + I_2$$

$$\therefore I_1 = 3 \text{ A}$$

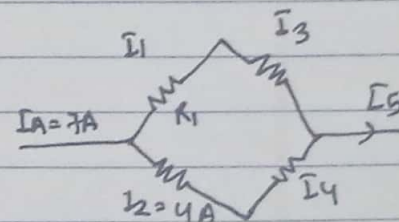

$$I_3 = I_1 = 3 \text{ A}$$

$$I_4 = I_2 = 4 \text{ A}$$

$$\therefore I_3 + I_4 = I_5 = 7 \text{ A}$$